

**Integrated Circuits and Applications**  
**Prof. Shaik Rafi Ahamed**  
**Department of Electronics and Electrical Engineering Indian Institute of**  
**Technology, Guwahati**

**Problem Solving**  
**Lecture – 13**  
**Examples on Instrumentation Amplifiers**

Ok. In the last lecture, we have discussed some of the problems, today, we will discuss some more practice problems. The next example is determine the output of the following circuit. This is basically a double integrator circuit. I have discussed about the single integrator, where this acts as a double integrator. This is inverting terminal, here we have capacitor, this is input voltage, this is the output voltage  $v_0$ , this is grounded. These values are  $R$ ,  $R$ ,  $C$ , this is  $\frac{C}{2}$ ,  $\frac{C}{2}$ ,  $\frac{R}{2}$ .

So, you have to find out the expression for the output of the circuit. Let us call this current as  $I_i$ , this current as  $I_1$ , this current as  $I_2$ , this current as  $I_3$ . If I assume that the op-amp is ideal, then this also will be at a same ground potential of this positive terminal. So, this will acts as a virtual ground.

So, if I consider the circuitry from  $v_i$  to this ground, this will be something like this is  $v_i$ , this is  $I_i$ , this is capacitor and then this resistor also will be grounded. These two points are grounded, because this point is this point which is virtual ground, this is virtual ground. This is  $v_i$ , this is  $I_i$ , I want the expression for  $I_i$  in terms of  $v_i$ . So, you can take this total impedance as  $Z$ . So,  $Z$  is nothing but these two will be in parallel in series with this.

This is  $Z = R + R \parallel \frac{1}{sC} = R + \frac{R \times \frac{1}{sC}}{R + \frac{1}{sC}} = R + \frac{R}{1+sRC} = \frac{R+sR^2C+R}{1+sRC} = \frac{sR^2C+2R}{1+sRC}$ . This is the total impedance of the circuit and we know that  $v_i = ZI_i \Rightarrow I_i = \frac{v_i}{Z} = v_i \frac{[1+sRC]}{[sR^2C+2R]}$ . This is expression for  $I_i$ . Now, what is the expression for  $I_1$ ? This  $I_1$ , there is a current division. This total current is  $I_i$ ; a part of this current flows through the capacitor, and the remaining part will through the resistor.


So, we know the expression for the current division circuit. So, the output through this resistor  $I_1$  is equal to total current  $I_i$  into opposite impedance divided by this impedance R resistance R. So, from current division formula  $I_1 = I_i \frac{\frac{1}{sC}}{R + \frac{1}{sC}} = \frac{I_i}{(1+sRC)}$ . This is equal to  $I_i$

times  $SC$   $SC$  will get cancel  $\frac{1}{SRC}$ . If I substitute this  $I_i$  here what will be  $I_1$ ?  $I_1 = \frac{[1+SRC]}{[SR^2C+2R]} \frac{v_i}{(1+SRC)} = \frac{v_i}{SR^2C+2R} = I_2$ . You can see that this  $I_1$  flows through the feedback path also because the current here is 0 because the operational amplifier is ideal this current is 0. So, the entire  $I_1$  will flows through this. So, this is also equal to  $I_2$ . Yes, I will call as equation 1.

Then I will consider the circuitry at the output side from here to this virtual ground. So, what will be this  $I_3$  now? Similar to this  $I_i$  we have considered from input side from here to here this was ground. Now, from here to this output side this output side if I consider. So,  $v_o$  is the voltage, and this  $I_3$  we have to find out. So, you have to find out this  $v_o$  in terms of  $I_3$  if I compute this impedance of this entire feedback path.

What is the impedance of this path? If I know this impedance, simply  $v_o = Z'I_3$ .

(Refer to the slide at 08:41)

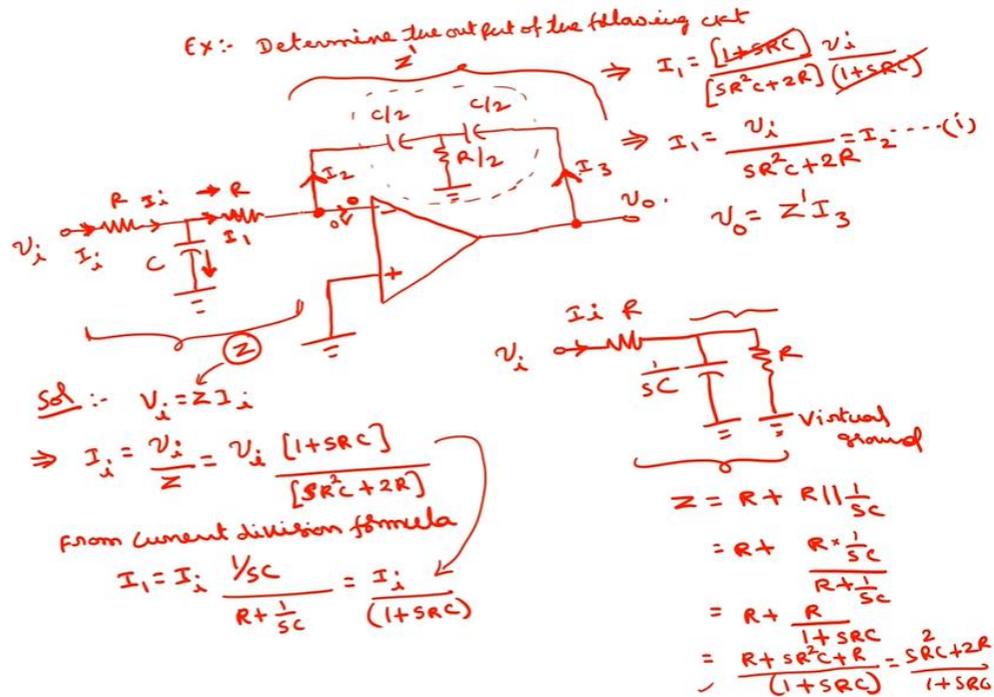

Here this  $Z'$  I am calling as this impedance. This you call as  $Z$  here, you have used similarly I will call this one as  $Z'$ . So, what is  $Z'$ ?  $Z'$  is this is at ground potential. So, what will be this equivalent circuit? This is the output  $v_o$ . This is the current  $I_3$ , and here you have one capacitance, one resistor, and one capacitance. This is also almost at the

ground. This is virtual ground now.

This is  $\frac{R}{2}, \frac{C}{2}, \frac{C}{2}$ , but in the S domain, this  $\frac{C}{2}$  becomes  $\frac{1}{SC/2} = \frac{2}{SC}$ . So, this entire impedance we are calling as  $Z'$ . So, what is  $Z'$ ?  $Z' = \frac{2}{SC} + \frac{2}{SC} \parallel \frac{R}{2} = \frac{2}{SC} + \frac{\frac{2}{SC} \times \frac{R}{2}}{\frac{2}{SC} + \frac{R}{2}} = \frac{2}{SC} + \frac{2R}{(SRC+4)} = \frac{2(SRC+4)+2SRC}{SC(SRC+4)} = \frac{4SRC+8}{SC(SRC+4)} = \frac{4(SRC+2)}{SC(SRC+4)}$ .

This is only  $Z'$ . What is  $v_o$ ?  $v_o = Z' I_3 \Rightarrow I_3 = \frac{SC(SRC+4)}{4(SRC+2)} v_o$ . You can call this as equation 2. Now, we have to find out this  $I_2$  because I have already derived the expression for the  $I_2$  this is equation 1.

Now, from this  $I_3$  also I will derive the expression for this  $I_2$ . So, that I can equate these two to find out the output  $v_o$ . Again, here, this current division this  $I_3$ , this is  $I_3$ , is divided into this resistor as well as this capacitor, but the current through this capacitor is in opposite direction. This is  $I_2$  we are taking. So, we will take minus sign. So, if you want  $I_2$ , this is equal to  $I_3$  into because we are going to find out the current through the capacitor  $\frac{C}{2}$ . You have to take the opposite impedance or resistance  $\frac{R}{2}$  divided by total impedance.

What will be expression for  $I_2$  in terms of  $I_3$ ? From current division formula,  $I_2$  is equal to minus  $I_3$  because now the direction is opposite to that of the current flow through the capacitor times you have to find out the current through this capacitor this one. So, you have to take the opposite impedance or resistance  $\frac{\frac{R}{2}}{\frac{R}{2} + \frac{SC}{2}}$ , here is equal to  $-\frac{SRC}{SRC+4} \times I_3$ . If I substitute this  $I_3$  here, what will be  $I_2$ ?  $I_2 = \frac{-SC(SRC+4)}{4(SRC+2)} \times \frac{SRC}{(SRC+4)} v_o = \frac{-S^2RC^2}{4(SRC+2)} v_o$ . This is the expression for  $I_2$ , I call as equation 3 and I have already derived the expression for the  $I_2$  here.

Now, we can equate this equation 1 and equation 3,  $I_2 = \frac{v_i}{SR^2C+2R} = \frac{-S^2RC^2}{4(SRC+2)} v_o$ ,  $v_o$  is here also. So, now, here, if I take in this denominator or if I take as common,  $\frac{v_i}{R(SRC+2)} = \frac{-S^2RC^2}{4(SRC+2)} v_o$ . So, this SRC plus 2 SRC plus 2 get cancelled.

(Refer to the slide at 16:01)

$$v_o = z' I_3 \Rightarrow I_3 = \frac{v_o}{z'}$$

$$\Rightarrow I_3 = \frac{sc(src+4)}{4(src+2)} v_o \dots (ii)$$

from current division formula

$$I_2 = -I_3 \cdot \frac{R/2}{\frac{R}{2} + \frac{2}{sc}} = -\frac{src}{(src+4)} I_3$$

$$\therefore I_2 = -\frac{sc(src+4)}{4(src+2)} \frac{src}{(src+4)} v_o$$

$$= -\frac{s^2 rc^2 v_o}{4(src+2)} \dots (iii)$$

$$I_2 = \frac{v_i}{\frac{R}{s^2 rc^2 + 2R}} = \frac{-s^2 rc^2 v_o}{4(src+2)}$$

$$= \frac{v_i}{R[src+2]} = \frac{-s^2 rc^2 v_o}{4[src+2]}$$

$\frac{1}{sc/2} = \frac{2}{sc} \quad z'$

$z' = \frac{2}{sc} + \frac{2}{sc} \parallel \frac{R}{2}$ 
 $= \frac{2}{sc} + \frac{2 \cdot \frac{R}{2}}{sc + \frac{R}{2}}$ 
 $= \frac{2}{sc} + \frac{2R}{(src+4)}$ 
 $= \frac{2(src+4) + 2src}{sc(src+4)}$ 
 $= \frac{4src+8}{sc(src+4)} = \frac{4(src+2)}{sc(src+4)}$

So, what will be resultant?  $\frac{v_i}{R} = -\frac{s^2 RC^2}{4} v_o \Rightarrow v_o = \frac{-4}{s^2 RC^2} v_i$ . This is expression for the output of the circuit. So, we know that in the S domain, if you have  $\frac{1}{s}$ , this is integration. If I have  $\frac{1}{s^2}$ , this will be double integration. So, if I remove this  $S^2$  here in the S domain in the time domain, it becomes a double integration. So, in terms of the output,  $v_o(t) = \frac{-4}{R^2 C^2} \iint v_i(t) dt$ . So, this given circuit will acts as double integrator ok.

(Refer to the slide at 17:31)

$$\Rightarrow \frac{v_i}{R} = \frac{-s^2 RC^2 v_o}{4}$$

$$\Rightarrow v_o = \frac{-4}{s^2 R^2 C^2} v_i$$

$\frac{1}{s} = \int$   
 $\frac{1}{s^2} = \iint$

$$\Rightarrow v_o(t) = \frac{-4}{R^2 C^2} \iint v_i(t) dt$$

This is one of the important circuit. The next example is to find out the output voltage of a instrumentation amplifier. Consider the instrumentation amplifier given below with a common mode voltage of plus 3V DC and the differential voltage of 80mV peak sinusoidal wave. So, the given circuit is this instrumentation amplifier. This is  $50k\Omega$ . This is also  $50k\Omega$ , this is  $1k\Omega$ .

And, here we have a differential amplifier. This is the final output  $v_o$ , these are all input voltage. Now, here the input voltage is given as a differential voltage of 80mV peak and common mode voltage of 3V DC. This is a 40mV peak; this is another 40mV peak. Both together will be 80mV peak, and this is a common mode signal. So, these two are differential signals.

So, this is the given circuit. So, the problem is determine the voltages at different nodes. Let us call this as node A, this as node B, node C, node D and then finally, the output voltage  $v_o$ . Hence, you have to find out what is  $v_A$ ,  $v_B$ ,  $v_C$ ,  $v_D$  and  $v_o$ . If I call this input voltage here as  $v_{01}$  voltage, this as  $v_{02}$  voltage. Then what is the expression for  $v_{01}$ ? If I go with this loop, so, this voltage will be this is minus 2 plus if I take as plus voltage.


So, 3V this is also minus 2 plus. This is peak value of 40mV means  $+0.04\sin\omega t$  is this voltage, peak value is 40mV, this is 40mV, and it is given as sinusoidal. So,  $\sin\omega t$  and here also this will be plus with respect to ground. This is place we are going to measure this with respect to the ground.

So, plus 2 minus this is minus 2 plus minus 2 plus this is plus 2 minus. So, minus  $v_{01}$  is equal to 0. This is plus means with respect to ground. So, ground is minus. So, this will be plus 2 minus implies what is  $v_{01}$ ?  $v_{01} = [3 + 0.04\sin\omega t]V$ ; this is so many volts.

Similarly, if I take this KVL in this loop, what is  $v_{02}$ ?  $v_{02}$  will be this will be place with respect to ground. This is minus 2 plus. If I take it as plus, this is plus 2 minus. This is also plus 2 minus. These two will be minus this is  $3V - 0.04\sin\omega t - v_{01} = 0$ , implies what is  $v_{02}$ ?  $v_{01} = [3 - 0.04\sin\omega t]Volts$ . So, we have determined this  $v_{01}$  and  $v_{02}$ , but we have to find out  $v_A$ ,  $v_B$ ,  $v_C$ ,  $v_D$  and final output  $v_o$ . How to find out  $v_A$ ? If I assume that this current is I flows in this direction, this is I because here the current is 0 because you are assuming that the op-amp is ideal. So, whatever the current that is coming from here, this I, the entire I will flows through this  $1k\Omega$  resistor because the current here is 0. Similarly, whatever the current that is coming here this entire current flows through this  $50k$  resistor because this current is 0. So, what will be expression for  $v_A$  now? This is  $v_{01}$  means because of the ideal op-amp, the voltage at inverting terminal is equal to the voltage at non inverting terminal. This is also  $v_{01}$ .

This is  $v_{02}$ , means this is also  $v_{02}$ . This current is 0, but voltage here is  $v_{02}$ . So, this voltage here is  $v_{01}$  here or here and this I want to find out  $v_A$ , this current direction is this one is plus minus. This  $v_{01}$  is plus with respect to the ground, which is minus. So, you are coming from minus to plus  $v_{01}$  minus to plus this  $i$  into  $50k$  and this is plus to minus. So, what is  $v_A$ ?  $v_A = v_{01} + 50k\Omega \times i$ , but what is  $i$ ?  $i$  is equal to this is  $v_{01}$ , this is  $v_{02}$  current direction is this.

(Refer to the slide at 26:51)

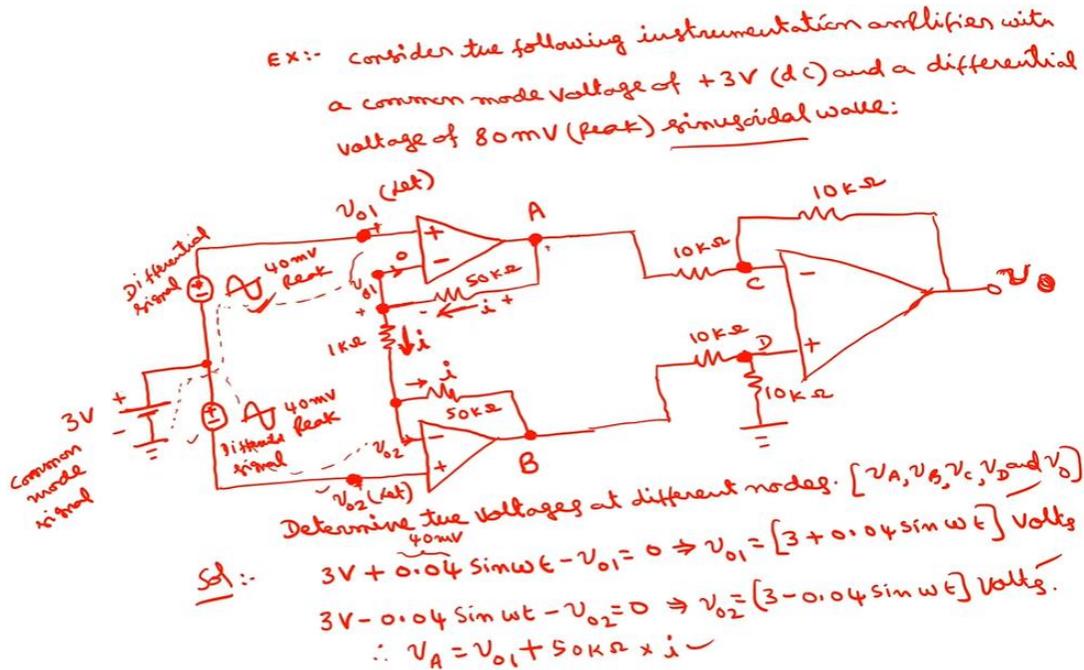

So,  $i = \frac{v_{01} - v_{02}}{1k\Omega}$ . What is  $v_{01}$  is this  $v_{02}$  this? So,  $i = \frac{3 + 0.04 \sin \omega t - 3 + 0.04 \sin \omega t}{1k\Omega} = 0.08 \sin \omega t$  mA.

This kilo I have taken to numerator that becomes milli amps this is the current. Therefore, what is  $v_A = v_{01} + 50 \times 10^3 \times 0.08 \sin \omega t \times 10^{-3} = v_{01} + 4 \sin \omega t = 3 + 0.04 \sin \omega t + 4 \sin \omega t = [3 + 4.04 \sin \omega t]$  volts. These two get cancelled 50 into 0.01 becomes 4.

So, implies  $v_A = [3 + 4.04 \sin \omega t]$  volts. This is the voltage at node A. Similarly, node B, what is  $v_B$ ? This is  $v_{02}$  and this current direction is this. This is minus 2 plus, this is plus 2 minus, this is plus 2 minus. So, this  $v_B = v_{02} - 50k\Omega \times i$ ,  $i$  is this, and  $v_{02}$  is this. This is equal to  $v_{02} = 3 - 0.04 \sin \omega t - 50 \times 10^3 \times 0.08 \sin \omega t \times 10^{-3} = [3 - 4.04 \sin \omega t]$  volts. This is mA. So, many volts. This is  $v_B$ . Now, what is  $v_C$ ? What is  $v_D$ ? What is  $v_O$ ? What is  $v_D$ ? From here, this is  $v_B$ , and this is voltage divider. This is

$v_B$ , and here, 10k, 10k, and this is the point where we are taking  $v_D$ . So, what is  $v_D$ ?  
 $v_D = v_B \times \frac{10k}{20k} = \frac{v_B}{2} = 1.5 + 2.02\sin\omega t$ . This is  $v_D$  and also  $v_C$  because this half amp is ideal. The voltage at inverting and non inverting are the same.

So,  $v_C$  and  $v_D$  both are same. So, implies  $v_C = v_D = 1.5 + 2.02\sin\omega t$ . Now, the last one is final output  $v_0$ .

We can see that what is this circuit from here to here. This we have already studied in the previous lectures. So, because this, all the 4 resistors are equal. So, output  $v_0$  is given by this voltage minus this voltage. This is positive is  $v_B$  negative is  $v_A$ . So, this is  $v_0 = v_B - v_A$  because these resistors are equal  $R_2$  by  $R_1$  into  $v_B$  minus  $v_A$ , but  $R_2$  is equal to  $R_1$ .

(Refer to the slide at 33:41)

$\therefore v_0 = -8.08 \sin\omega t \text{ volts}$

$$i = \frac{v_{o1} - v_{o2}}{1k\Omega} = \frac{3 + 0.04 \sin\omega t - 3 + 0.04 \sin\omega t}{1k\Omega}$$

$$= 0.08 \sin\omega t \text{ mA}$$


$$\therefore v_A = v_{o1} + 50 \times 10^3 \times 0.08 \sin\omega t \times 10^{-3}$$

$$= v_{o1} + 4 \sin\omega t = 3 + 0.04 \sin\omega t + 4 \sin\omega t$$

$$\Rightarrow v_A = [3 + 4.04 \sin\omega t] \text{ volts}$$

$$v_B = v_{o2} - 50k\Omega \times i$$

$$= 3 - 0.04 \sin\omega t - 50 \times 10^3 \times 0.08 \sin\omega t \times 10^{-3}$$
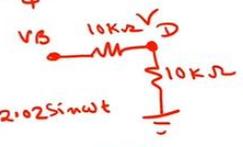
$$\Rightarrow v_B = [3 - 4.04 \sin\omega t] \text{ volts}$$


$$v_D = v_C = \frac{10k}{20k} v_B = \frac{v_B}{2} = 1.5 + 2.02 \sin\omega t$$

$$\Rightarrow v_C = v_D = [1.5 + 2.02 \sin\omega t] \text{ volts} \Rightarrow v_0 = v_B - v_A$$

So, this is  $v_B - v_A$  simply. This is different circuit or subtractor, which we have already studied subtractor. So, what is  $v_0$  implies  $v_0 = v_B - v_A$ . So, if I subtract  $v_A$  from this  $v_B$ , 3 3 get cancelled will get minus therefore,  $v_0 = -8.08\sin\omega t \text{ volts}$ . So, this is about this circuit. Next, we will discuss some of the examples on finding the CMRR of a given circuit. Thank you.