

**Integrated Circuits and Applications**  
**Prof. Shaik Rafi Ahamed**  
**Department of Electronics and Electrical Engineering Indian Institute of**  
**Technology, Guwahati**

**Problem Solving**  
**Lecture – 14**  
**Examples on Instrumentation CMRR Computation**

Ok. In the last few lectures, we are discussing about some of the practicing problems. Today we will discuss some more problems on finding the *CMRR* of a given circuit. So, first, I will find out the *CMRR* of a instrumentation amplifier. We have find out the *CMRR* of differential amplifier. So, that time, I told that the *CMRR* of instrumentation amplifier is greater than that of the differential amplifier, which is one of the advantage of instrumentation amplifier. Today, we will derive the expression for the *CMRR* of instrumentation amplifier.

Find the *CMRR* of the following instrumentation amplifier. See the circuit diagram given. Basically, two voltage followers followed by a differential amplifier. This is the output  $R_3$   $R_4$   $R_3$  then this  $R_4$ .

Here we are going to apply the input signal. This is  $R_2$   $R_2$  this is  $R_1$   $R_1$ . Then here we will be having two components one is differential signal, another is common mode signal. This is common mode signal. This can be plus or minus; also like in previous example, this was plus and minus. Now, I am taking minus plus. This can be of any type.


So, here I am going to apply  $\frac{v_d}{2}$  voltage differential voltage another  $\frac{v_d}{2}$  here total is  $v_d$ . So, you have to find out the common mode rejection ratio of this circuit *CMRR* is common mode rejection ratio. How efficiently this circuit rejects the common mode signal such as the noise? If I call this signal as  $v_{i1}$  input 1 this signal as  $v_{i2}$  this output as  $v_{o1}$  this as  $v_{o2}$ . So, what are the expressions for  $v_{i1}$ ,  $v_{i2}$ ,  $v_{o1}$ ,  $v_{o2}$ ? If I consider this  $v_{cm}$  this  $\frac{v_d}{2}$  this  $v_{i1}$ . So, what will be the loop? This  $v_{cm}$  is minus to plus this is  $v_{cm}$  this is, of course, grounded, and then this  $\frac{v_d}{2}$  is minus to plus then you have to find out this  $v_{i1}$  this is with respect to plus and minus this is  $v_{i1}$ .

So, what is KVL? This is minus to plus this is plus to minus this is plus to minus. If I take minus to plus as positive then this will be  $v_{cm}$  and this is plus to minus. So,  $v_{cm} - \frac{v_d}{2} - v_{i1} = 0 \Rightarrow v_{i1} = v_{cm} - \frac{v_d}{2}$ , whereas, to find out this,  $v_{i2}$ . So, what will be circuitry? This  $v_{cm}$  this  $v_d$  by 2. This  $v_{i2}$  similar type of the circuit you can have here. So, this is now  $v_{cm}$ .

This is plus-minus, and this is minus plus, and this is connected to  $v_{i2}$ . This is  $v_d$  by 2.

If I take minus to plus as positive this is plus to minus this is plus to minus this is minus to plus. You can see here minus to plus, then minus to plus, then this is plus to minus, this is also minus to plus this is minus to plus. If you go in this direction again, this is minus to plus. So, what will be this minus to plus if I take as  $v_{cm} + \frac{v_d}{2} - v_{i2} = 0 \Rightarrow v_{i2} = v_{cm} + \frac{v_d}{2}$ .

(Refer to the slide at 08:00)

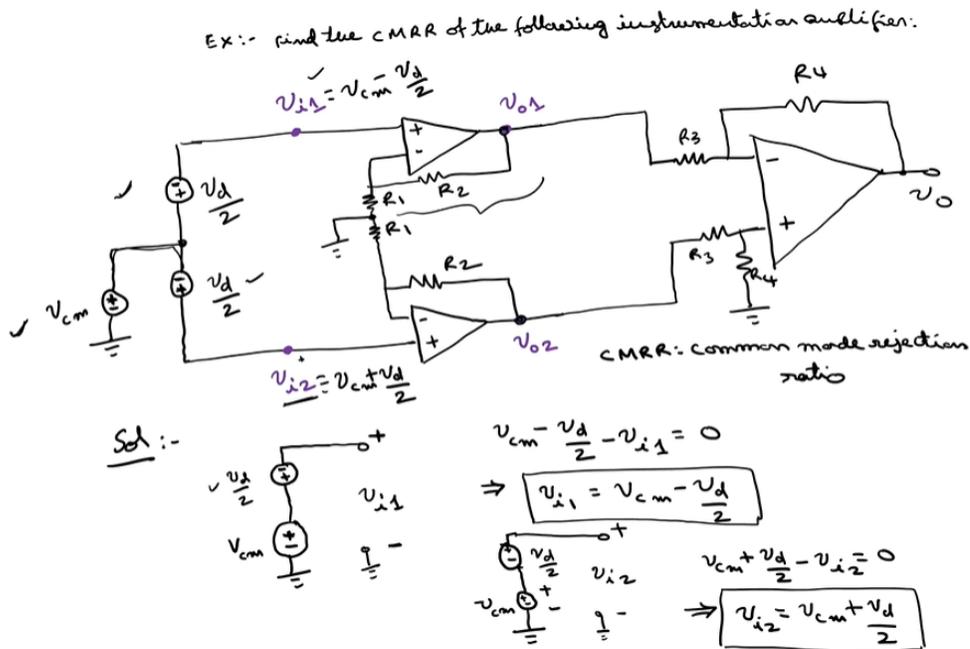

Now I have to find out this output voltages  $v_{o1}$   $v_{o2}$ . So, what is  $v_{o1}$ ? You can see that this circuit this circuit is nothing, but a non-inverting amplifier this is grounded. So, the gain is one plus feedback resistance by input resistance. So, if I draw the equivalent circuit of this one. So, you say positive terminal negative terminal we have these two ground these two this and at positive terminal we have  $v_{i1}$  this output is  $v_{o1}$ .

You can see that this is positive terminal is  $v_{i1}$ , and at negative terminal, we have feedback resistance  $R_2$  input resistance which is grounded is  $R_1$ , and output is  $v_{o1}$  this is  $R_1$  this is  $R_2$ . This is a standard non-inverting amplifier whose gain is  $(1 + \frac{R_2}{R_1})$ . So,  $v_{o1} = (1 + \frac{R_2}{R_1})v_{i1}$ , but what is  $v_{i1}$  from the previous circuit  $v_{cm} - \frac{v_d}{2}$ . So, this  $v_{o1} = (1 + \frac{R_2}{R_1})(v_{cm} - \frac{v_d}{2})$ . Similarly, what about  $v_{o2}$ ? The circuitry for  $v_{o2}$  is also similar type of

circuit.

Here at positive terminal we have  $v_{i2}$  negative terminal  $R_1$  is grounded  $R_2$  is feedback resistance output is  $v_{o2}$ . So, to find out  $R_2$ , the same circuit is there, but in place of  $v_{i1}$ , we have  $v_{i2}$ , and this is grounded. This is  $v_{o2} R_2 R_1$ . So,  $v_{o2} = (1 + \frac{R_2}{R_1})v_{i2}$ . Now, what is the difference between the  $v_{o2}$  and  $v_{o1}$ ? Because this is differential amplifier, the input that is applied to the non-inverting terminal is  $v_{o2}$ . So, you take the difference signal of  $v_{o2} - v_{o1}$

The differential output due to differential signal is  $v_{o2} - v_{o1} = (1 + \frac{R_2}{R_1})v_{i2} - (1 + \frac{R_2}{R_1})v_{i1} = (1 + \frac{R_2}{R_1})(v_{i2} - v_{i1})$ . What is  $v_{i2}$ ? Is  $v_{i2} = v_{cm} + \frac{v_d}{2}$  and what is  $v_{i1}$ ?  $v_{i1} = v_{cm} - \frac{v_d}{2}$ . What is  $v_{i2}$  minus  $v_{i1}$ ?  $v_{cm}$  will get cancelled this becomes  $\frac{2v_d}{2}$  or simply  $v_d$ . So, you see nothing but  $v_d$ . This is  $v_{o2} - v_{o1} = (1 + \frac{R_2}{R_1})v_d$ .

So, this will be the differential gain this is differential output differential input. So, whatever the factor of this one is differential gain. Therefore, differential gain  $A_d = 1 + \frac{R_2}{R_1}$ .

(Refer to the slide at 13:03)

$$v_{o1} = (1 + \frac{R_2}{R_1})v_{i1}$$

$$\Rightarrow v_{o1} = (1 + \frac{R_2}{R_1})(v_{cm} - \frac{v_d}{2})$$

$$\therefore v_{o2} = (1 + \frac{R_2}{R_1})v_{i2}$$



✓  $\therefore$  Differential output due to differential input signal is

$$v_{o2} - v_{o1} = (1 + \frac{R_2}{R_1})v_{i2} - (1 + \frac{R_2}{R_1})v_{i1}$$

$$= (1 + \frac{R_2}{R_1})(v_{i2} - v_{i1})$$

$$= (1 + \frac{R_2}{R_1})v_d$$

$\therefore$  Differential gain  $A_d = 1 + \frac{R_2}{R_1}$
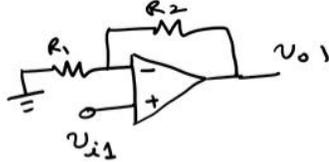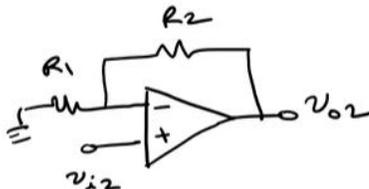
$$v_{o2} = v_{i2} (1 + \frac{R_2}{R_1})$$

$$v_{i2} = v_{cm} + \frac{v_d}{2}$$

$$v_{i1} = v_{cm} - \frac{v_d}{2}$$

$$v_{i2} - v_{i1} = v_d$$

Then you have to find out the common mode gain to find out the *CMRR*. So, what is common mode gain? This is differential output due to the differential input signal. Now, what is the output due to the common mode signal? Is nothing, but  $\frac{v_{o1}+v_{o2}}{2}$ , this is the output. This is equal to what is  $v_{o1}$  is this  $v_{o2}$  is this  $\frac{(1+\frac{R_2}{R_1})v_{i1}+(1+\frac{R_2}{R_1})v_{i2}}{2}$ . This is equal to  $\frac{1}{2}\left(1+\frac{R_2}{R_1}\right)(v_{i1}+v_{i2}) = \frac{1}{2}\left(1+\frac{R_2}{R_1}\right)\left(v_{cm}-\frac{v_d}{2}+v_{cm}+\frac{v_d}{2}\right) = \left(1+\frac{R_2}{R_1}\right)v_{cm}$ .

So, you will get this is simply  $\left(1+\frac{R_2}{R_1}\right)v_{cm}$ ,  $v_{cm}$  is the common mode signal. So, this is common mode gain. The output due to the common mode signal is equal to the common mode signal into whatever the factor that factor is common mode gain. Therefore, the common mode gain  $A_{cm} = 1 + \frac{R_2}{R_1}$ , and what is the differential gain we have obtained is also same. Therefore, the common mode rejection ratio is defined as  $CMRR = 20\log\left|\frac{A_d}{A_{cm}}\right|$  20 logarithm of modulus of AD by ACM. This is equal to  $20\log\left|\frac{A_d}{A_{cm}}\right|$ . Both are the same. So,  $20\log 1$ . So, this is simply 0dB. So, for the given circuit the *CMRR* is 0dB. So, this is not the good circuit. So, if *CMRR* is high, then it is a good circuit ok. So, this circuit is not a good circuit for the instrumentation amplifier.

(Refer to the slide at 15:39)

output due to common mode signal

$$\begin{aligned} \frac{v_{o1}+v_{o2}}{2} &= \frac{\left(1+\frac{R_2}{R_1}\right)v_{i1}+\left(1+\frac{R_2}{R_1}\right)v_{i2}}{2} \\ &= \frac{1}{2}\left(1+\frac{R_2}{R_1}\right)(v_{i1}+v_{i2}) \\ &= \frac{1}{2}\left(1+\frac{R_2}{R_1}\right)\left(v_{cm}-\frac{v_d}{2}+v_{cm}+\frac{v_d}{2}\right) \\ &= \left(1+\frac{R_2}{R_1}\right)v_{cm} \end{aligned}$$

Common mode gain  $A_{cm} = 1 + \frac{R_2}{R_1}$

$$\therefore CMRR = 20\log\left|\frac{A_d}{A_{cm}}\right| = 20\log 1 = 0\text{ dB}$$

Now, I will consider the second circuit and I will find out the  $CMRR$  and I am going to prove that the second circuit is having good  $CMRR$ . So, most of the practical applications uses the second type of the instrumentation amplifier.

So, the next example is find the  $CMRR$  of the following instrumentation amplifier. So, almost similar circuit with slight modification. So, this part is exactly same. This is output, this is  $R_3$   $R_3$   $R_4$   $R_4$ . Here you are going to take  $v_{i1}$ , this is  $v_{i2}$ , and here, we are going to connect a  $2R$  resistor,  $2R_1$  resistor.

Instead of having  $2R_1$  resistors in series and in between we have a ground. Now, we have  $2R_1$  resistor without any ground. The remaining connections are same. This is  $R_2$ , this is also  $R_2$ , and here this differential signal, this is another differential signal, and this is common mode signal. This is plus minus  $v_{cm}$ , this is minus plus minus plus, this is  $\frac{v_d}{2}$ , this is  $\frac{v_d}{2}$ .

Then we have already derived that this is  $v_{o1} = v_{cm} - \frac{v_d}{2}$ . This you have derived that  $v_{o2} = v_{cm} + \frac{v_d}{2}$ . But the output  $v_{o1}$  and  $v_{o2}$  will be different now because here the connection has been changed. If I assume that this current is  $I$ , the same current flows through. If this current is  $I$ , the same current flows through this, the same current flows to this because the operational amplifiers are ideal.


So, the current through this terminal is 0, current through this terminal is 0. So, whatever the current coming from here, so this will go to this, this will go through this  $2R_1$ , then the same current will flow through this  $R_2$  resistor, here current is 0. So, now, what will be expression for  $v_{o1}$ ,  $v_{o2}$ ? For that first, I will find out current  $i$ . This is the direction of the  $i$ . So, this voltage is nothing but  $v_{o1}$ .

The second assumption of the ideal operational amplifier, the voltage at non-inverting terminal is equal to voltage at the inverting terminal. So, this is  $v_{o1}$  means this is also  $v_{o1}$ . So, the voltage at non-inverting terminal of second operational amplifier is  $v_{o2}$ , means the voltage at inverting terminal also  $v_{o2}$ . Now, this is the current, this is  $v_{o1}$ , this is  $v_{o2}$ , direction of the current is from  $v_{o1}$  to  $v_{o2}$ . So, what is expression for  $i = \frac{v_{o1} - v_{o2}}{2R_1}$ .

Now, knowing this  $v_{o1}$ , how to find out? This is  $v_{i1}$ ,  $v_{i2}$ , this is  $v_0$ , this is input currents. So, this is  $v_{i1} - v_{i2}$ . So, to find out  $v_{o1}$  from  $v_{i1}$ , so what is the KVL? This is  $v_{i1}$ , and this is plus to minus, and this  $v_{i1}$  is with respect to this, this is plus with respect to ground, this is with respect to ground. So, this is something like we have this  $v_{i1}$  with respect to ground, this is  $v_{i1}$  plus minus, then we have the resistor, then you are going to take the output here with respect to ground, this is plus minus and the direction of this current

here is this means this is plus, this is minus, this is  $R_2$ , this is  $v_{o1}$ , this is  $v_{i1}$ . So, what is the relation between the  $v_{i1}$ ,  $v_{o1}$  and  $R_2$ ? Minus to plus if I take as positive, so  $v_{i1}$  and this is also minus to plus. So, the current is  $v_{i1} + iR_2 - v_{o1} = 0 \Rightarrow v_{o1} = v_{i1} + iR_2$ . But what is  $i$ ?  $i = \frac{v_{o1} - v_{o2}}{2R_1}$ . So,  $v_{o1} = v_{i1} + (\frac{v_{o1} - v_{o2}}{2R_1})R_2$ , what is  $v_{i1}$ ?  $v_{cm} - \frac{v_d}{2}$ . What is  $v_{i1}$  minus  $v_{i2}$ ?  $v_{i1}$  is this one. So,  $v_{i1} - v_{i2} = v_{cm} - \frac{v_d}{2} - v_{cm} - \frac{v_d}{2} = -v_d$ . So, implies what is  $v_{o1}$  final expression?  $v_{o1} = v_{cm} - \frac{v_d}{2} + \frac{R_2}{2R_1}(-v_d)$ .

(Refer to the slide at 23:39)

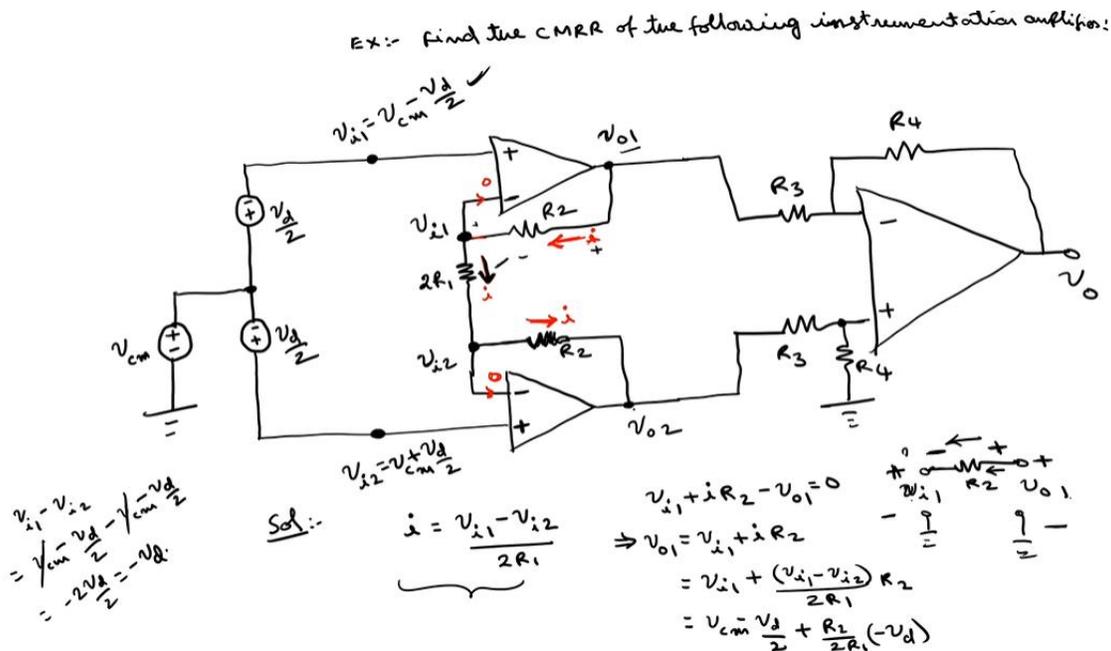

And if you take this  $\frac{v_d}{2}$  as common, this is  $v_{o1} = v_{cm} - \frac{v_d}{2}(1 + \frac{R_2}{R_1})$ . This is one expression for  $v_{o1}$ . Similarly, how to find out the expression for  $v_{o2}$ ? So, you can consider now this path, this resistance, this current, this is  $v_{i2}$  and this is  $v_{o2}$ . So, if I write a similar type of the circuit here,  $v_{i2}$   $R_2$   $v_{o2}$ ,  $v_{o2}$ , this is  $v_{i2}$  passing through the circuit  $R_2$ , and here we are taking the output with respect to ground plus-minus this is  $v_{o2}$ .


And what is the direction of the current in this  $R_2$ ? This is the direction of the current from  $v_{i2}$  to  $v_{o2}$ , this is  $I$  means this is plus this is minus. So, what is the relation between  $v_{i2}$   $v_{o2}$  and the voltage drop across  $R_2$ ? Minus to plus if I take as positive  $v_{i2}$ , the voltage drop across  $R_2$  is plus to minus. So,  $v_{i2} - iR_2 - v_{o2} = 0 \Rightarrow v_{o2} = v_{i2} - iR_2$ . This is equal to  $v_{i2}$  is nothing, but  $v_{cm} + \frac{v_d}{2}$  minus I have derived as this  $i = \frac{v_{i1} - v_{i2}}{2R_1}$ .

So,  $v_{i1} - v_{i2} = v_d$ . So,  $v_{o2} = v_{cm} + \frac{v_d}{2} + \frac{R_2}{2R_1}(v_d) = v_{cm} + \frac{v_d}{2}(1 + \frac{R_2}{R_1})$ . This is equal to  $v_{cm}$ . If we take as common, this will be  $1 + \frac{R_2}{R_1}$ . So, this is the expression for  $v_{o2}$  you can write as 2. This is equation for  $v_{o1}$ . Now we have to take  $v_{o2} - v_{o1}$ . This is differential output due to differential signal, and the factor of  $v_d$  is differential gain.

So, this is  $v_{o2}$  minus  $v_{o1}$ . So, the factor of  $v_d$  is the differential gain. So, what is  $v_{o2} - v_{o1}$ ?  $v_{o2} - v_{o1} = v_{cm} + \frac{v_d}{2}(1 + \frac{R_2}{R_1}) - v_{cm} + \frac{v_d}{2}(1 + \frac{R_2}{R_1}) = v_d(1 + \frac{R_2}{R_1})$ , implies this will be the common mode gain  $A_d = (1 + \frac{R_2}{R_1})$ .

(Refer to the slide at 28:25)
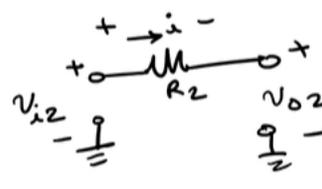
$$\begin{aligned} \therefore v_{o1} &= v_{cm} - \frac{v_d}{2} - \frac{R_2}{2R_1} v_d \\ &= v_{cm} - \frac{v_d}{2} (1 + \frac{R_2}{R_1}) \dots (i) \end{aligned}$$



$$\begin{aligned} v_{i2} - iR_2 - v_{o2} &= 0 \\ \Rightarrow v_{o2} &= v_{i2} - iR_2 \\ &= v_{cm} + \frac{v_d}{2} - \left(\frac{v_{i1} - v_{i2}}{2R_1}\right)R_2 \end{aligned}$$

$$\begin{aligned} \Rightarrow v_{o2} &= v_{cm} + \frac{v_d}{2} - \frac{R_2}{2R_1} (-v_d) \\ &= v_{cm} + \frac{v_d}{2} (1 + \frac{R_2}{R_1}) \dots (ii) \end{aligned}$$

$$\begin{aligned} \checkmark v_{o2} - v_{o1} &= v_{cm} + \frac{v_d}{2} (1 + \frac{R_2}{R_1}) - v_{cm} + \frac{v_d}{2} (1 + \frac{R_2}{R_1}) \\ &= (1 + \frac{R_2}{R_1}) v_d \end{aligned}$$

$\xrightarrow{\hspace{10em}} A_d = 1 + \frac{R_2}{R_1}$

Similarly, in order to obtain the common mode gain you have to take the sum of this by 2, therefore,  $\frac{v_{o1} + v_{o2}}{2} = \frac{\{v_{cm} - \frac{v_d}{2}(1 + \frac{R_2}{R_1})\} + \{v_{cm} + \frac{v_d}{2}(1 + \frac{R_2}{R_1})\}}{2} = v_{cm}$ .

Here what is the factor of  $v_{cm}$  which is the common mode gain is unity. So, we got  $A_d = (1 + \frac{R_2}{R_1})$  and  $A_{cm} = 1$  ACM as unity. Therefore, what is  $CMRR = 20 \log \left| \frac{A_d}{A_{cm}} \right| =$

$20\log\left(1 + \frac{R_2}{R_1}\right)$ . So, there are two circuits. For the first circuit, we have got  $CMRR$  as 0; for the second circuit, we have got as  $20\log\left(1 + \frac{R_2}{R_1}\right)$ . So, which one is better circuit because this  $CMRR$  is greater than 0dB this is better circuit this is better circuit for instrumentation amplifier.

(Refer to the slide at 30:06)

$$\frac{v_{o1} + v_{o2}}{2} = \frac{\left\{v_{cm} - \frac{v_d}{2}\left(1 + \frac{R_2}{R_1}\right)\right\}}{2} + \frac{\left\{v_{cm} + \frac{v_d}{2}\left(1 + \frac{R_2}{R_1}\right)\right\}}{2}$$

$\uparrow$   $= v_{cm}$        $A_{cm} = 1$   
 $A_d = 1 + \frac{R_2}{R_1}$

$\therefore CMRR = 20 \log \left| \frac{A_d}{A_{cm}} \right|$

$= 20 \log \left( 1 + \frac{R_2}{R_1} \right)$

So, both the circuits are instrumentation amplifiers only, but the second circuit is a better circuit in terms of the common mode rejection ratio because it can reject the common mode signals in efficient manner. What is the reason for that one? You can see this from this if I take  $v_{o1}$  what is the gain for this  $v_{cm}$  is  $1 + \frac{R_2}{R_1}$  even in this  $v_{o2}$  also if I substitute this  $v_{cm} + \frac{v_d}{2}$  the gain is  $1 + \frac{R_2}{R_1}$ . So, the gain for the common mode signals in first circuit is  $1 + \frac{R_2}{R_1}$  that is undesired common mode signal is normally the noise. So, for which we should not provide any gain, but the first circuit is providing a gain of  $1 + \frac{R_2}{R_1}$  for the common mode signal.

Interestingly if I take the second circuit. So, this is the output for the  $v_{o1}$ . So, what is the gain for  $v_{cm}$ ? Unity. So, whatever this common mode signal here the same  $v_{cm}$  is obtained at the output also without any gain whereas, in case of the first circuit this  $v_{cm}$  at the input after the first stage this is appearing as  $1 + \frac{R_2}{R_1}$  times  $v_{cm}$ . So, because this circuit amplifies the common mode signals also. So, the common mode rejection ratio is less whereas, the second circuit does not amplify this  $v_{cm}$  here the output is also  $v_{cm}$ .

So, this second circuit will be having better  $CMRR$ . So, this is about this two instrumentation amplifier circuits and the corresponding  $CMRR$ . I will take one problem on the slew rate. Suppose a sinusoidal signal is having a slew rate of  $60V/\mu\text{sec}$ . What is the highest frequency that attains a  $20V(P-P)$  output without distortion?  $20V$  peak to peak signal means peak value will be  $10V$ . So, what is the type of the input signal? The output signal that we have to obtain is  $20V$  peak to peak signal  $v_o = 10\sin\omega t$ .

What will be the highest frequency of this one? That will obtain this output voltage with  $10V$  peak signal without any distortion ok. For that we have to find out a  $\frac{dv_o}{dt}$ . This is,  $\frac{dv_o}{dt} = 10\omega\cos\omega t$ , and what is the maximum value of this  $\frac{dv_o}{dt}$ ? Of course, minus and I am not taking this I want the magnitude only maximum value maximum value of  $\cos$  is unity. So,  $|\frac{dv_o}{dt}|_{\text{max}} = 10\omega$ , is defined as slew rate. This is equal to  $60 \times 10^6$ . So, it  $10\omega_{\text{max}}$ , you have to find out the maximum value of the frequency which can give  $10V$  peak value of the output sinusoidal signal is equal to  $60 \times 10^6 \Rightarrow 2\pi f_{\text{max}} = 60 \times 10^6 \Rightarrow f_{\text{max}} = \frac{3}{\pi} \times 10^6 \text{Hz} \approx 45.5\text{kHz}$ .

(Refer to the slide at 35:49).

Ex:- Let sinusoidal signal has a slew rate of  $60V/\mu\text{sec}$   
 what is the highest frequency that attains a 20V(P-P)  
 output without distortion?

Sol:-

$$v = 10\sin\omega t$$



$$\left| \frac{dv_o}{dt} \right| = 10\omega \cos\omega t$$

$$\left| \frac{dv_o}{dt} \right|_{\text{max}} = 10\omega = \text{slew rate} = 60 \times 10^6$$

$$10\omega_{\text{max}} = 60 \times 10^6$$

$$\Rightarrow 2\pi f_{\text{max}} = 6 \times 10^6$$

$$\Rightarrow f_{\text{max}} = \frac{3}{\pi} \times 10^6 \text{Hz} \approx 45.5\text{kHz}$$

So, we know that the slew rate for a given output without any distortion, we can find out the maximum input frequency, or we can do in another way also. For a given maximum frequency, what is the maximum output that can be obtained without any distortion? This we have already discussed in the previous lectures.

So, these are some problems. Next, we will discuss about some specialized applications of the operational amplifiers, such as filters, oscillators, etcetera. Thank you.