

Course name: EMI /EMC and Signal Integrity: Principles, Techniques and Applications.

Professor name: Prof. Amitabha Bhattacharya


Department name: Electronics and Electrical Communication Engineering

Institute name: IIT Kharagpur

Week :07

Lecture 33: Development of Multi Conductor Transmission Line Equation

Welcome to the 33rd lecture on of the course on EMIMC and Signal Integrity Principles, Techniques and Applications. We were discussing three conductor line, we have found its equivalent circuit for a section of the line in the last class. Now, today we will derive or develop its transmission line equation. So, we can go to the previous class that this is the line. So, here let me do one more thing that let me put the two nodes, one is this node let me call A and this node let me call B. Now, here what I will do simply that I will find between the two conductor at a time we will write the KVL and KCL equations. So, you see that if first I will write across the generator reference loop. So, that means the topmost and the bottom most conductor along that if I take KVL equation then you see that I can take it suppose I am starting from here then $V_g \Delta z$ minus $R_g \Delta z$ minus $L_g \Delta z \frac{dI_g}{dt}$ minus V_g at $z + \Delta z$ plus $R_g \Delta z$ into I_g at $z + \Delta z$ plus I_r at z that should be equal to 0.

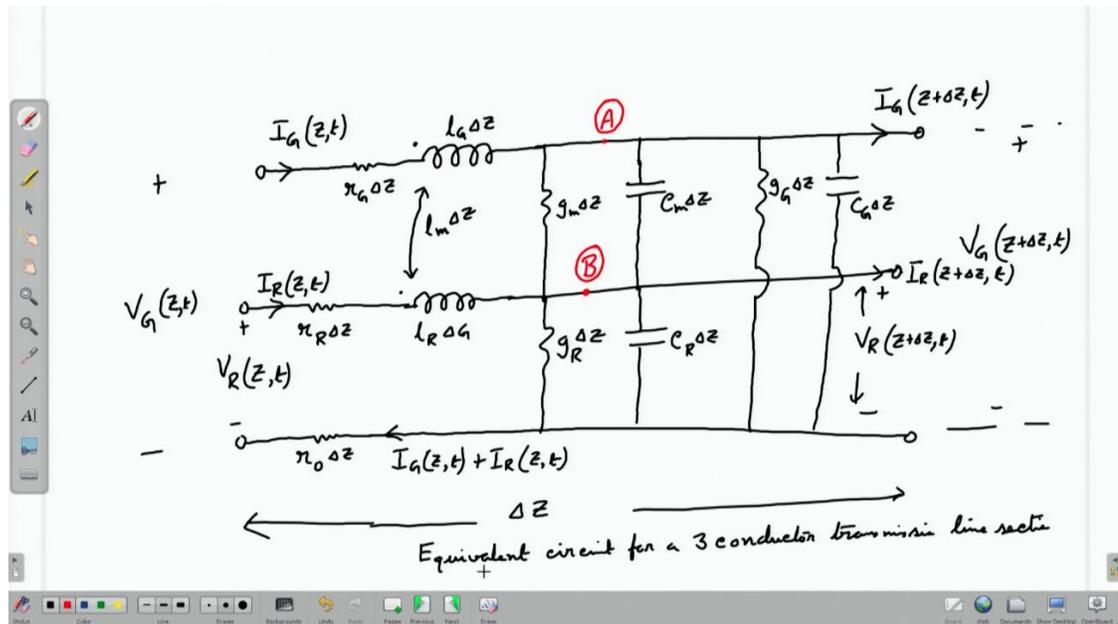

So, let me write that. So, writing KVL across the generator reference loop. So, what I said now I will write. You can see it $V_g(z,t) - I_g(z,t) R_g \Delta z - L_g \Delta z \frac{\partial I_g(z,t)}{\partial t} - I_r(z,t) R_r \Delta z - L_r \Delta z \frac{\partial I_r(z,t)}{\partial t} - V_g(z+\Delta z, t) = 0$. Then the loop $V_g(z,t) - I_g(z,t) R_g \Delta z - L_g \Delta z \frac{\partial I_g(z,t)}{\partial t} - I_r(z,t) R_r \Delta z - L_r \Delta z \frac{\partial I_r(z,t)}{\partial t} - V_g(z+\Delta z, t) = 0$. So, $R_g \Delta z + L_g \frac{\partial}{\partial t} + R_r \Delta z + L_r \frac{\partial}{\partial t}$ then $I_g(z,t) + I_r(z,t)$. So, that is equal to 0. Now before writing other equations let me make it you know that I will have to bring the two voltages together. So, I can write for $V_g(z,t) - V_g(z+\Delta z, t) = -R_g I_g \Delta z - L_g \frac{\partial I_g}{\partial t} \Delta z - R_r I_r \Delta z - L_r \frac{\partial I_r}{\partial t} \Delta z$. So, I can write for $V_g(z,t) - V_g(z+\Delta z, t) = -R_g I_g \Delta z - L_g \frac{\partial I_g}{\partial t} \Delta z - R_r I_r \Delta z - L_r \frac{\partial I_r}{\partial t} \Delta z$. Now, if I take limit Δz goes to 0. So, I can write $\frac{\partial V_g}{\partial z} = -R_g I_g - L_g \frac{\partial I_g}{\partial t} - R_r I_r - L_r \frac{\partial I_r}{\partial t}$. So let me call this equation, equation number 1.

LECTURE 33 : DEVELOPMENT OF MULTI CONDUCTOR TRANSMISSION LINE EQUATION

Writing KVL across the generator-reference loop,

$$V_g(z,t) - I_g(z,t) R_g \Delta z - L_g \Delta z \frac{\partial I_g(z,t)}{\partial t} - I_r(z,t) R_r \Delta z - L_r \Delta z \frac{\partial I_r(z,t)}{\partial t} - V_g(z+\Delta z, t) = 0$$

$$\Rightarrow \frac{V_g(z+\Delta z, t) - V_g(z,t)}{\Delta z} = -R_g I_g(z,t) - L_g \frac{\partial I_g(z,t)}{\partial t} - R_r I_r(z,t) - L_r \frac{\partial I_r(z,t)}{\partial t}$$

$$\Rightarrow \frac{\partial V_g}{\partial z} = -(R_g + R_r) I_g - L_g \frac{\partial I_g}{\partial t} - L_r \frac{\partial I_r}{\partial t}$$

Now how many such equations will be there you see this one loop I have taken along the generator reference another loop is there the receptor reference. So, there also one KVL will come then there are two nodes as you have seen A B in node A I can write a KCL equation in node B I will write a KCL equation. So, there will be four such equations let me write them one by one in the same fashion. So, this KVL along receptor reference loop. So, that will give me V_r just exactly similar to the previous one. You keep the

equivalent circuit in front of you till I am doing that that makes it easier instead of every time going there and looking at it. This is now I g because I am writing in difference of the mutual one that will give me that will be based on I g. So, again I can I will do that V r.

$V_r(z+\Delta z, t) - V_r(z, t)$ and I will divide by Δz . So, that will be outside separate then I will take the Δz goes to 0 because this will be as online. So, I will get another equation that will be $\frac{\partial V_r}{\partial z}$ is equal to minus $R_0 I_g$ minus R_r plus $R_0 I_r$ minus $L_m \frac{\partial I_g}{\partial t}$ minus $L_r \frac{\partial I_r}{\partial t}$. This will be my equation number 2. Now, I will write KCL along at node a. So, you see at node a the incoming currents are $I_g(z, t)$ then the outgoing current is I_g . Now, in the there is a current g_m I am assuming that this is positive. So, there will be the through $g_m \Delta z$ there will be a current that will depend on the difference of voltages between V_g and V_r . Then through c_m also there will be a outgoing current that will be $\frac{\partial}{\partial t} (V_g - V_r)$ then through g_g there will be a current Δz that will depend on the voltage here $V_g(z+\Delta z, t)$ plus Δz and then through c_g again there will be a voltage that is $\frac{\partial}{\partial t} (V_g + \Delta z)$. So, I can write that that there is one in going incoming current to node a all others are outgoing current. So, I can write as $I_g(z, t)$ is equal to $I_g(z+\Delta z, t)$ plus $g_m \Delta z (V_g - V_r)$ plus $c_m \Delta z \frac{\partial}{\partial t} (V_g - V_r)$ plus $g_g \Delta z V_g(z+\Delta z, t)$ plus $c_g \Delta z \frac{\partial}{\partial t} (V_g + \Delta z)$.

KVL along reception-reference loop,

$$V_R(z, t) - R_0 \Delta z I_R(z, t) - L_r \Delta z \frac{\partial I_R(z, t)}{\partial t} - I_m \Delta z \frac{\partial I_G(z, t)}{\partial t} - V_R(z + \Delta z, t) - R_0 \Delta z \{ I_G(z, t) + I_R(z, t) \}$$

$$\frac{\partial V_R}{\partial z} = -R_0 I_G - (R_0 + R_r) I_R - L_m \frac{\partial I_G}{\partial t} - L_r \frac{\partial I_R}{\partial t} \dots (2)$$

KCL at node (A)

$$I_G(z, t) = I_G(z + \Delta z, t) + g_m \Delta z \{ V_G(z + \Delta z, t) - V_R(z + \Delta z, t) \} + c_m \Delta z \frac{\partial}{\partial t} \{ V_G(z + \Delta z, t) - V_R(z + \Delta z, t) \} + g_g \Delta z V_G(z + \Delta z, t) + c_g \Delta z \frac{\partial}{\partial t} \{ V_G(z + \Delta z, t) \}$$

No more current now again the same technique that $I_g(z, t) - I_g(z + \Delta z, t)$ keep it one side all others another side divide by Δz then take limit of Δz to 0 that will give you a $\frac{\partial I_g}{\partial z}$ is equal to $-g_g + g_m V_g + g_m V_r - c_g \frac{\partial V_g}{\partial t} + c_m \frac{\partial V_r}{\partial t}$. So, this will be your equation number 3. Similarly, the last one KCL at node b in similar fashion you can write that $I_r(z, t) - I_r(z + \Delta z, t) + g_r \Delta z V_r(z + \Delta z, t) + c_r \Delta z \frac{\partial V_r(z + \Delta z, t)}{\partial t} + g_m \Delta z \{V_r(z + \Delta z, t) - V_g(z + \Delta z, t)\} + c_m \Delta z \frac{\partial}{\partial t} \{V_r(z + \Delta z, t) - V_g(z + \Delta z, t)\}$ will be $I_r(z, t) - I_r(z + \Delta z, t) + g_r \Delta z V_r(z + \Delta z, t) + c_r \Delta z \frac{\partial V_r(z + \Delta z, t)}{\partial t} + g_m \Delta z \{V_r(z + \Delta z, t) - V_g(z + \Delta z, t)\} + c_m \Delta z \frac{\partial}{\partial t} \{V_r(z + \Delta z, t) - V_g(z + \Delta z, t)\}$ So, again taking the two currents to one side taking limit you will get the fourth equation $\frac{\partial I_r}{\partial z}$ is equal to $g_m V_g - g_r V_r + g_m V_r + c_m \frac{\partial V_g}{\partial t} - c_r \frac{\partial V_r}{\partial t}$. So, this will be your equation number 4.

$$\frac{\partial I_g}{\partial z} = -(g_g + g_m) V_g + g_m V_r - (c_g + c_m) \frac{\partial V_g}{\partial t} + c_m \frac{\partial V_r}{\partial t} \quad \dots (3)$$

KCL at node B,

$$I_r(z, t) - I_r(z + \Delta z, t) + g_r \Delta z V_r(z + \Delta z, t) + c_r \Delta z \frac{\partial V_r(z + \Delta z, t)}{\partial t} + g_m \Delta z \{V_r(z + \Delta z, t) - V_g(z + \Delta z, t)\} + c_m \Delta z \frac{\partial}{\partial t} \{V_r(z + \Delta z, t) - V_g(z + \Delta z, t)\}$$

$$\frac{\partial I_r}{\partial z} = g_m V_g - (g_r + g_m) V_r + c_m \frac{\partial V_g}{\partial t} - (c_r + c_m) \frac{\partial V_r}{\partial t} \quad \dots (4)$$

So, four equations you have got and this partial differential equations can be written by showing explicitly all the terms we can write it in more compact form and for that we can just write it as in matrix form oh sorry $\frac{\partial}{\partial z} [V(z,t)] + [G] [V(z,t)] - [L] \frac{\partial}{\partial t} [I(z,t)] = -[R] [I(z,t)] - [C] \frac{\partial}{\partial t} [V(z,t)]$. The first two KVL equations can be written like this and second two KCL equations can be just written like this. Just see the four equations we can easily write them in this matrix form. You see such elegant where what is $V(z,t)$? $V(z,t)$ is nothing, but a vector $V(z,t)$. Similarly, what is $I(z,t)$ vector $I(z,t)$ that is also a vector it is $I(z,t)$. So, in matrix form the four equations are just written as two equations like our two wire transmission line system and what is this four matrix R, L, G, C you can just look at those equation 1 2 3 4 and that will tell you the per unit length length parameters.

$$\frac{\partial}{\partial z} [V(z,t)] = -[R] [I(z,t)] - [L] \frac{\partial}{\partial t} [I(z,t)]$$

$$\frac{\partial}{\partial z} [I(z,t)] = -[G] [V(z,t)] - [C] \frac{\partial}{\partial t} [V(z,t)]$$

where $[V(z,t)] = \begin{bmatrix} V_g(z,t) \\ V_r(z,t) \end{bmatrix}$

$$[I(z,t)] = \begin{bmatrix} I_g(z,t) \\ I_r(z,t) \end{bmatrix}$$

So, the per unit length parameter matrix matrices are first is what is our R matrix? This is your where is equation 1. So, you see what is R matrix? Can I say that R matrix the first one the it will be a 2 by 2 matrix the r_{11} will be R_g plus r_{naught} r_{12} will be r_{naught} then go to the second equation r_{21} will be r_{naught} r_{22} will be r_r plus r_{naught} . So, write that. So, r is R_g plus r_{naught} r_{naught} this is r_{naught} r_r plus r_{naught} and its unit is in ohms per meter. Similarly, there will be a 2 by 2 L matrix. So, let us again go to equation 1. So, what is L matrix? The L_{11} will be L_g L_{12} will be L_m L_{21} will be L_m L_{22} will be L_r . So, I will write that that it is L_g L_m L_r and what is its unit in Henry

per meter then there will be g matrix conductance matrix. So, they will come from the third and fourth equation. So, third equation where is this is third equation. So, what will be g_{11} g_{12} g_{21} g_{22} g_{r} plus g_m . Now, here it will be g_{11} is g_g plus g_m , but g_{12} will be minus g_m because in general we have taken the equation as minus g into V g t . You see that our equation is minus g into s o those which are positive terms they will become negative in the per unit length parameters. So, I can easily write that g is equal to g_g plus g_m this is minus g_m this is also minus g_m g_r plus g_m . And what is its unit it will be Siemens per meter conductance unit is Siemens. So, per unit length parameter is Siemens per meter and finally, there will be per unit length capacitance matrix. So, let us see it will also come from equation third and fourth also it is minus c . So, remember so where is 3 yes. So, it is c_{11} will be c_g plus c_m c_{12} will be minus c_m c_{21} will be minus c_m c_{22} will be c_r plus c_m . So, it is c_g plus c_m minus c_m it is minus c_m it is c_r plus c_m mean farad per meter. So, this sorry this equation is actually called MTL equation or multi conductor transmission line equation. For our case 3 conductor case it is becoming these if it is 4 conductor it will be a these vectors will be 3 I Z T will also be 3 and the per unit length parameters they will be 3 by 3 matrices. So, there will be 9 terms in that etcetera. So, sorry multi conductor transmission line. So, MTL M T L equations multi conductor. So, this is the equation for multi conductor transmission line equation. So, we have derived it as I said that from the same approach as we take for 2 conductor line these things were derived.

per unit length parameter matrices are

$$[R] = \begin{bmatrix} r_g + r_o & r_o \\ r_o & r_r + r_o \end{bmatrix} \text{ in } \Omega/\text{m}$$

$$[L] = \begin{bmatrix} l_g & l_m \\ l_m & l_r \end{bmatrix} \text{ in } \text{H}/\text{m}$$

$$[G] = \begin{bmatrix} g_g + g_m & -g_m \\ -g_m & g_r + g_m \end{bmatrix} \text{ in } \text{S}/\text{m}$$

$$[C] = \begin{bmatrix} c_g + c_m & -c_m \\ -c_m & c_r + c_m \end{bmatrix} \text{ in } \text{F}/\text{m}$$

MTL Eq:

$$\frac{\partial}{\partial z} \begin{bmatrix} V(z,t) \\ I(z,t) \end{bmatrix} = - \begin{bmatrix} R & L \\ G & C \end{bmatrix} \begin{bmatrix} V(z,t) \\ I(z,t) \end{bmatrix}$$

where $\begin{bmatrix} V(z,t) \\ I(z,t) \end{bmatrix} = \begin{bmatrix} V_G(z,t) \\ V_R(z,t) \\ I_G(z,t) \\ I_R(z,t) \end{bmatrix}$

MULTI CONDUCTOR TRANSMISSION LINE EQUATIONS

And now in the next class we will move from here we will have to find various things finally, also we will this is the transmission line equations then we will have to find the for 3 conductor again we will have to derive the per unit length parameters of various 3 conductor lines and then from that we will move to a model of a crosstalk. So, with that I finish today's lecture we have done a great job today that multi conductor transmission line is completely new to you. So, that we have derived from basic principles of KVL and KCL. Thank you.