

Course name: EMI /EMC and Signal Integrity: Principles, Techniques and Applications.
 Professor name: Prof. Amitabha Bhattacharya
 Department name: Electronics and Electrical Communication Engineering
 Institute name: IIT Kharagpur
 Week :09
 Lecture 41: Determination of Crosstalk (continued)

Welcome to the lecture of the course on EMI EMC and Signal Integrity Principles Techniques and Applications. In the last class we have determined I_0 that means, the current at the receptor at the source end or at the near end. Now using reciprocity we are doing a trick to find easily from that expression the current in the far end. So, with that replacement, if we put that into equation 12 we get. So, this is our equation 13 where we have got the value of I_{SL} I_L . So, if we expand this equation 12 and 13 we get the terminal currents that is I_0 and I_2 and then we can easily solve for it because these are two simultaneous equations. Now to simplify the notations what we will do we will put some simplification because every time this $\cos \beta L$ and $\sin \beta L$ by βL is coming. So, for them we assume that let P is equal to $\cos \beta L$ and S is equal to $\sin \beta L$ by βL .

LECTURE 41: DETERMINATION OF CROSSTALK (CONTD 2)

Egn (12) \rightarrow

$$\left[\cos \beta L (\tilde{Z}_L + \tilde{Z}_S) + \frac{\sin \beta L}{\beta L} \{ j\omega L + [\tilde{Z}_S] j\omega L [\tilde{Z}_L] \} \right] [\tilde{I}(x)]$$

$$= - \left[\cos \beta L [I_2] + \frac{\sin \beta L}{\beta L} [\tilde{Z}_S] (j\omega L [c]) \right] [\tilde{V}_L] + [\tilde{V}_S]$$

----- (13)

Let $p = \cos \beta L$
 $s = \frac{\sin \beta L}{\beta L}$

So, we can write it now by expanding the see these there are Z L matrix Z S matrix L matrix C matrix Z L V L matrix V S matrix. So, these we already know because when we draw the circuit we have determined them . So, we will now make use of those definitions. So, P is P is P into this Z L. So, in place of Z L I may write R L 0 these are given earlier you may recall R f e plus Z L plus Z S. So, Z S matrix is R S 0 0 R m e plus S 0 0 R m e plus J omega L then L matrix. So, that we know is L g L m L m L r plus R S what was the term ah L plus Z S. So, Z S is again R S 0 0 R m e then J omega L then C matrix. So, C g plus C m minus C m minus C m C r plus C m and then Z L is C L again. So, into Z L is R L 0 0 R f e into I L. So, I L is nothing, but I g L m L r and I R L. So, this will be equal to minus minus you see P into I 2. So, I can write P 0 0 P plus S into Z S Z S is R S 0 0 R m e into J omega L. So, this is J omega L C J omega L C matrix. So, C g plus C m minus C m minus C m C r plus C m into V L. Now, our V L is there is no excitation at the load end. So, it is 0 0 plus we have V S. So, V S is we are energizing the generator we are not energizing the receptors. So, V S 0.

From (13) →

$$\begin{bmatrix} p \\ 0 \end{bmatrix} \left(\begin{bmatrix} R_L & 0 \\ 0 & R_{FE} \end{bmatrix} + \begin{bmatrix} R_S & 0 \\ 0 & R_{NE} \end{bmatrix} \right) + s \left\{ j\omega L \begin{bmatrix} L_g & L_m \\ 0 & L_r \end{bmatrix} + \begin{bmatrix} R_S & 0 \\ 0 & R_{NE} \end{bmatrix} j\omega L \begin{bmatrix} C_g + C_m & -C_m \\ -C_m & C_r + C_m \end{bmatrix} \right\} \begin{bmatrix} R_L & 0 \\ 0 & R_{FE} \end{bmatrix} \begin{bmatrix} \tilde{I}_g(x) \\ \tilde{I}_r(x) \end{bmatrix}$$

$$= - \begin{bmatrix} p & 0 \\ 0 & p \end{bmatrix} + s \begin{bmatrix} R_S & 0 \\ 0 & R_{NE} \end{bmatrix} j\omega L \begin{bmatrix} C_g + C_m & -C_m \\ -C_m & C_r + C_m \end{bmatrix} \begin{bmatrix} 0 \\ 0 \end{bmatrix} + \begin{bmatrix} \tilde{V}_S \\ 0 \end{bmatrix}$$

So, this from this we can just do one more simplification some matrix terms take you see the first one if I take I can make I can take P common and from that with a smaller third bracket I can write R L plus R S 0 0 R f e plus R m e plus S J L J omega L. So, J omega L L matrix is L g L m L m L r plus. So, R S 0 0 R m e into here we are clubbing this C matrix into the J L matrix. So, we are getting C g plus C m into R L minus C m into R f e minus C m R L into R m e minus C m R L plus C m into R f e. I think it is write another third bracket will come yes another I think third bracket will come then we have I g L I R L and right side you see that the first term is fully 0. So, we are left with only P S and

0. We can further simplify that P we can take inside this. So, P R L plus R S into 0 into P R a P plus R m e plus J omega L S L g L m L r plus R m e plus R m e plus J omega L g L m L m L r plus R S R L C g plus C m minus C m into R f e minus C m R L into R f e minus R S R a P C m minus R m e R L C m R m e R a P minus R m e minus R f e minus R m e R a P C r plus C m and this one is C r plus C m. Then the second bracket should end the third bracket should be 0. Then multiplied with this I g L I R L is equal to 0.

$$\begin{bmatrix} P [R_L + R_S & 0 \\ 0 & R_{FE} + R_{NE}] \end{bmatrix} + s j \omega X \left\{ \begin{bmatrix} L_g & L_m \\ L_m & L_R \end{bmatrix} + \begin{bmatrix} R_S & 0 \\ 0 & R_{NE} \end{bmatrix} \begin{bmatrix} (C_g + C_m) R_L & -C_m R_{FE} \\ -C_m R_L & (C_R + C_m) R_{FE} \end{bmatrix} \right\}$$

$$\begin{bmatrix} \tilde{I}_g(x) \\ \tilde{I}_R(x) \end{bmatrix} = \begin{bmatrix} \tilde{V}_S \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} P (R_L + R_S) & 0 \\ 0 & P (R_{FE} + R_{NE}) \end{bmatrix} + j \omega X S \left\{ \begin{bmatrix} L_g & L_m \\ L_m & L_R \end{bmatrix} + \begin{bmatrix} R_S R_L (C_g + C_m) & -R_S R_{FE} C_m \\ -R_{NE} R_L C_m & R_{NE} R_{FE} (C_R + C_m) \end{bmatrix} \right\}$$

$$\begin{bmatrix} \tilde{I}_g(x) \\ \tilde{I}_R(x) \end{bmatrix} = \begin{bmatrix} \tilde{V}_S \\ 0 \end{bmatrix}$$

we are doing one by one matrix multiplication. So, that is why so many steps are coming. So, we have R a P L m minus R S R a P C m L m minus R m e R L C m minus R f e minus C m L r plus R m e R f e C r plus C m. Now, we will do another one. One more this addition needs to be done. So, for P R L plus R S plus J omega L S plus R L G plus R S R L C G plus C m minus J omega L S L m minus J omega L m minus J omega L G plus R S R a P C m J omega L S L m minus R f e. R plus R m e R a P C r plus C m into I g L plus R m e R f e into R f e into R f e into I R L is equal to your P S 0. So, let us also give this is P S 0. Let us give it some name. Suppose I call it f 1. No, I need not call it any equation. So, actually this will give me two simultaneous equation. So, one for I g L, another is for one for this V S, another is for this 0.

$$\begin{bmatrix} P(R_L + R_S) & 0 \\ 0 & P(R_{FE} + R_{NE}) \end{bmatrix} + j\omega \begin{bmatrix} L_G + R_S R_L (C_n + C_m) & L_m - R_S R_{FE} C_m \\ L_m - R_{NE} R_L C_m & L_R + R_{NE} R_{FE} (C_n + C_m) \end{bmatrix} \begin{bmatrix} \tilde{I}_G(s) \\ \tilde{I}_R(s) \end{bmatrix} = \begin{bmatrix} \tilde{V}_S \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} P(R_L + R_S) + j\omega \{L_G + R_S R_L (C_n + C_m)\} \\ j\omega \{L_m - R_{NE} R_L C_m\} \end{bmatrix} \begin{bmatrix} \tilde{I}_G(s) \\ \tilde{I}_R(s) \end{bmatrix} = \begin{bmatrix} \tilde{V}_S \\ 0 \end{bmatrix}$$

So, that let us do then we will name them. So, from the first row we get that P. So, P R S plus R L plus J omega L S R S R L G plus C m G plus C m G plus C m G plus I g L C g plus C m plus L g I g L plus J omega L S R L G plus R f e into R f e into R f e into L s L m minus C m R S R f e I R L is equal to V S. Now, we have got J omega L S and J omega L S L m minus C m R L R m e I g L S minus C m g L plus P R n e plus R f e plus J omega L S R f e. Now, we have got J omega L S plus R f e plus J omega L S plus R f e plus J omega L S plus R L is equal to 0. So, these two follows from this one, this one into I g L minus this one into I R L is equal to V S and this one into I g L plus this one into I R L is equal to 0. So, these two I want to name. So, let us name something what is coming to my mind f e. So, there are two simultaneous equations in the unknowns I g L and I R L.

$$\begin{bmatrix} P \{R_S + R_L\} + j\omega \{R_S R_L (C_n + C_m) + L_G\} \\ j\omega \{L_m - C_m R_S R_{FE}\} \end{bmatrix} \begin{bmatrix} \tilde{I}_G(s) \\ \tilde{I}_R(s) \end{bmatrix} = \tilde{V}_S \quad \dots (I)$$

$$\begin{bmatrix} j\omega \{L_m - C_m R_L R_{NE}\} \\ P \{R_{NE} + R_{FE}\} + j\omega \{R_{NE} R_{FE} (C_n + C_m) + L_R\} \end{bmatrix} \begin{bmatrix} \tilde{I}_G(s) \\ \tilde{I}_R(s) \end{bmatrix} = 0 \quad \dots (II)$$

one I have given V_1 I f 1. So, let me call this is an important thing that V_{fe} we have determined. So, this I will say that we have achieved something that V_{fe} is this. So, the cross talk at the far end we have determined in the next class we will determine the V_{ne} that is cross talk at the near end. Thank you.

$$V_{FE} = R_{FE} I_R(x) = \frac{j\omega \times S \{C_m R_L R_{NE} - I_m\} R_{FE} \tilde{V}_S}{\Delta_1}$$

91