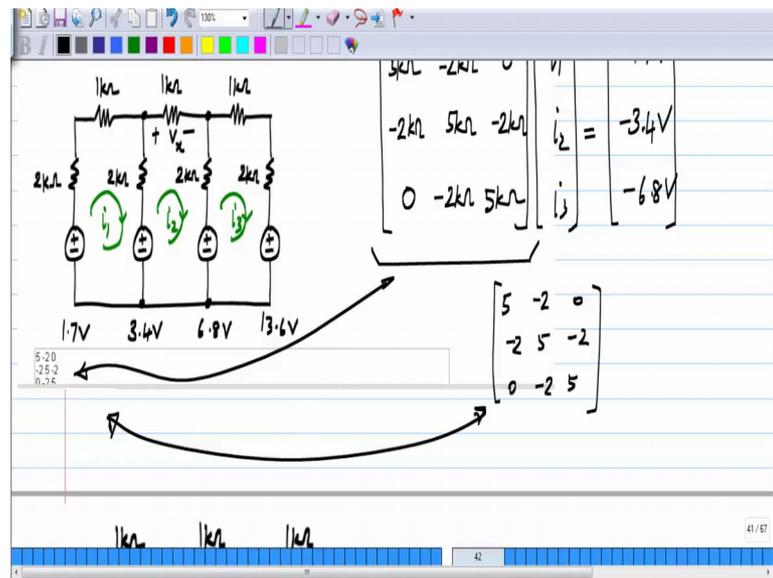


Basic Electrical Circuits
Dr Nagendra Krishnapura
Department of Electrical Engineering
Indian Institute of Technology Madras

Lecture - 71

Now, we will discuss solution to the assignment on units 9 and 10 on mesh analysis.

(Refer Slide Time: 00:05)




So, the first question is to set up mesh analysis equations for this particular circuit. And, so in this case we have only resistors and voltage sources, so it is the easiest case for mesh analysis. We will have three meshes, which are already given to you I 1, I 2, I 3 the mesh currents are already given and this first coefficient here is the sum of all resistance in this mesh, which is 2 kilo ohms plus 1 kilo ohms plus 2 kilo ohm, which is 5 kilo ohms.

This entry is negative of the resistance common to mesh 1 and mesh 2, which is 2 kilo ohms to have minus 2 kilo ohms. And finally, this entry is the resistance common to meshes 1 and 3 and there is no such resistor, so this is 0. And the second mesh, the total resistance is 5 kilo ohms that appears here along the diagonal, then this entry is negative of resistance common to mesh 1 and 2, which is this 2 kilo ohms, so we have minus 2 kilo ohms and this entry is negative of resistance common to this and that mesh, which is again minus 2 kilo ohms.

Finally, for the third mesh the total resistance is 5 kilo ohms, which appears here along the diagonal, then we have 2 kilo ohms, which is common to meshes 2 and 3 and nothing common to meshes 1 and 3. Anyway by symmetric, we have already filled these, so we can fill these and on the right side, we will have the total voltage rise in each mesh and that is in the first mesh if you look at this direction, we have a voltage rise of 1.7, voltage drop of 3.4, so we will have minus 1.7 volts, second mesh voltage rise of 3.4, voltage fall of 6.8.


So, the net voltage fall of 3.4 volts and the third one voltage rise of 6.8, voltage fall of 13.6, so a total voltage rise of minus 6.8 volts. In any case, what you are asked in this is resistance matrix which is given here, you should omit the units and enter only the numerical values in kilo ohms, which is 5, minus 2, 0, minus 2, 5, minus 2 and 0 minus 2 5, so that is the answer.

(Refer Slide Time: 03:27)

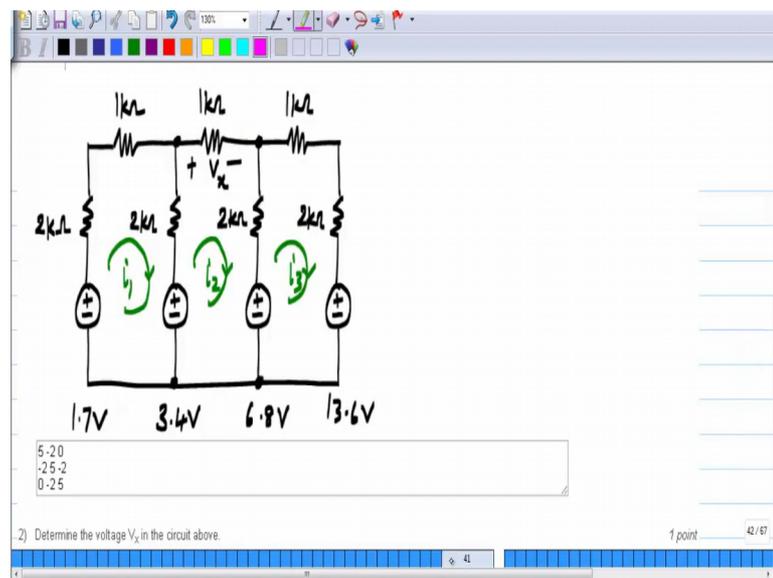

Now, in the next question it is the same circuit and you are asked to determine the voltage V_x . Voltage V_x is this one, which means that basically whatever we set up earlier we have to solve. So, in this we have to find V_x , so we have to solve this.

(Refer Slide Time: 03:59)

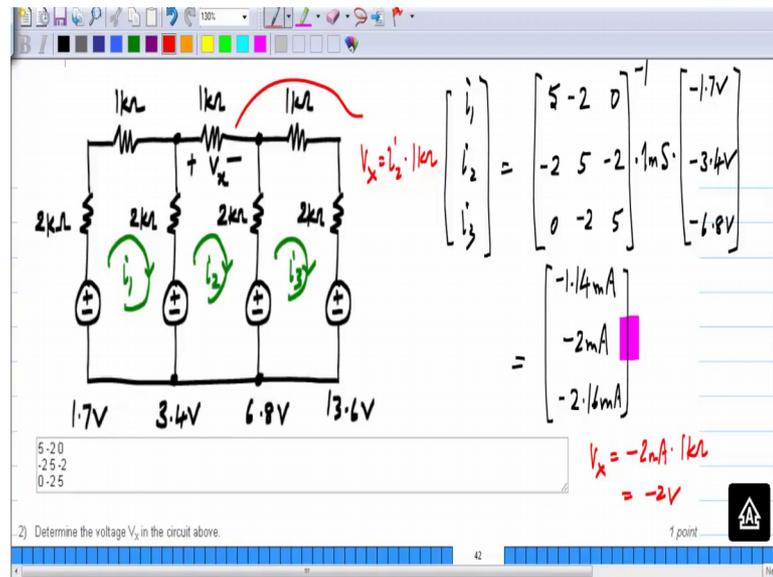

So, first define the current vector which is basically and by the way, the entries here had units of kilo ohms, so the inverse has units of Millisiemens. So, I will multiply the whole thing by 1 Millisiemen and this has to be multiplied by the source vector, which was minus 1.7 volts minus 3.4 volts and minus 6.8 volts. And if you do this, the answer comes out to be minus 1.14 milli amp minus 2 milli amp and minus 2.16 milli amp.

Now, clearly you can see that this V_x is I_2 times 1 kilo ohm, I_2 is the current flowing through this resistor, which belongs only to mesh number 2 and its resistance is 1 kilo ohm and I_2 we see is minus 2 milli amperes. So, V_x is minus 2 milli amperes times 1 kilo ohms equals minus 2 volts.

(Refer Slide Time: 05:31)

5-20
-25-2
0-25

2) Determine the voltage V_x in the circuit above. 1 point
(The answer should be the numerical value of the voltage in volts(V), e.g.
If your answer is 1.5V, write 1.5
If your answer is -5V, write -5
If your answer is 30mV, write 0.03 or 3e-2 or 30e-3 etc.)

-2

3) Setup mesh analysis equations for the circuit below. The mesh currents are identified in the circuit. Enter the resistance [R] matrix in the space provided. 1 point
below, one row on each line. e.g. the 3x3 identity matrix should be entered as

1 0 0
0 1 0
0 0 1

• Do not have any space at the start of the line

42 / 67

Handwritten notes: $V_x = -2 \text{ mA} \cdot 1 \text{ k}\Omega = -2 \text{ V}$

And you can see that, minus 2 volts is the right answer.

(Refer Slide Time: 05:41)

The [R] matrix entries should be the numerical values in kilohms(k Ω) and should be rounded to one decimal place. i.e.
If the answer is 1.5k Ω , write 1.5
If the answer is -5k Ω , write -5
Do not use decimal places if the answer happens to be an integer. i.e. Do not write 5.0 for 5.

Handwritten notes: $i_x = i_3 - i_2$, $i_1 \cdot 3 \text{ k}\Omega - i_2 \cdot 1 \text{ k}\Omega = 1.5 \text{ V} = 1 \text{ k}\Omega (i_3 - i_2)$

$$\begin{bmatrix} 3 & -2 & 1 \\ -1 & 3 & -1 \\ -1 & 1 & -2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 0.5 \\ -2 \\ -2 \end{bmatrix}$$

Matrix entries: $3 \text{ k}\Omega$, $-2 \text{ k}\Omega$, $1 \text{ k}\Omega$, $-1 \text{ k}\Omega$, $3 \text{ k}\Omega$, $-1 \text{ k}\Omega$, $-1 \text{ k}\Omega$, $1 \text{ k}\Omega$, $-2 \text{ k}\Omega$

Matrix entries: 3 , -2 , 1 , -1 , 3 , -2 , 1 , 0 , -2 , 1 , 0 , -1 , 3

Matrix entries: 0.5 , -2 , -2

Matrix entries: 3 , -2 , 1 , -1 , 3 , -2 , 1 , 0 , -2 , 1 , 0 , -1 , 3

43 / 67

Now, again there is another question, where you have to set up mesh analysis equations and the only difference from before is that, before we had only voltage sources, independent voltage sources and resistors. Now, we have independent voltage sources, a current dependent voltage source and resistors. So, now, this current here is 1 kilo ohm times I_x and I_x is defined in that direction. You can clearly see that I_x equals i_3 minus

i_2 , I_x is flowing upwards in this branch and that is equal to i_3 , which is defined to be flowing upwards and i_2 , which is flowing downwards.

So, essentially here we have an additional voltage drop, which is 1 kilo ohm times i_3 minus i_2 , so that is the voltage drop. So, now, this we have i_3 and i_2 , so if we look at this mesh excluding this, we will get some resistances and if we include this, the coefficients of those currents i_3 and i_2 will be modified; that is if you write down the mesh equation here, we will get i_1 times 3 kilo ohms, which is the total resistance in this mesh and we have minus 1 kilo ohm, because of this resistance which is common to meshes 1 and 2 and there is nothing common to meshes 1 and 3.

This will be equal to the total voltage rise, which is half a volt, which is the voltage rise minus a voltage drop, which is that one 1 kilo ohms times i_3 minus i_2 . Now, of course, this is also an unknown, so it will go to the other side, so what happens is that, in the first equation the right hand side source vector will be this 0.5 volts which is due to the independent source and on the left side, the coefficient of i_1 is 3 kilo ohms, the coefficient of i_2 is minus 1 kilo ohm and plus 1 kilo ohm from there, which is minus 2 kilo ohms.

Finally, is basically plus 1 kilo ohm times i_3 when you transfer this to the other side. And similarly, if you look at the second row I will first write the conventional terms, which basically are the total mesh resistance 3 kilo ohm, which appears here and resistance common to meshes 1 and 2, which is 1 kilo ohm, which appears there and the distance common to meshes 2 and 3, which is again 1 kilo ohm, which appears over there.

But, additionally we also have a voltage rise of 1 kilo ohm times i_3 minus i_2 , on the left hand side we count voltage drops, so that becomes 1 kilo ohm for i_2 and minus 1 kilo ohm for i_3 and on the right hand side, we have the independent voltage rise, which is equal to minus 2 volts, because we have a voltage drop of 2 volts. So, now, of course, we have to combine these, this one remains as minus 1 kilo ohm, this becomes 4 kilo ohm and this becomes minus 2 kilo ohms.

Finally, the third mesh it is conventional, because we have only voltage sources and resistors. So, the total mesh resistance of 3 kilo ohms appears here and whatever is common to meshes 2 and 3 appears here with a negative sign and whatever is common to

meshes 1 and 3, which is really nothing appears there. And on the right hand side we have the total voltage raised, which is plus 2 volts minus 4 volts, which is minus 2 volts.

So, if you look at just resistance matrix this part it will be 3 minus 2 1 in the first row minus 1 4 minus 2 in the second row 0 minus 1 3 in the third row and it has units of kilohms and in the answer you are required to entire the numerical values in the kilo ohms. So, this is the answer.

(Refer Slide Time: 11:19)


The screenshot shows a circuit with three meshes. Mesh 1 contains a 1kΩ resistor and a 0.5V voltage source. Mesh 2 contains a 1kΩ resistor, a 2V voltage source, and a dependent current source labeled $1k\Omega \cdot I_x$. Mesh 3 contains a 1kΩ resistor and a 4V voltage source. Handwritten notes include the resistance matrix $\begin{bmatrix} 3 & -2 & 1 \\ -1 & 4 & -2 \\ 0 & -1 & 3 \end{bmatrix}$ and the source vector $\begin{bmatrix} -2V \\ -2V \\ -2V \end{bmatrix}$. The resulting mesh currents are $i_1 = -0.2 \text{ mA}$, $i_2 = -1.06 \text{ mA}$, and $i_3 = -1.02 \text{ mA}$. Below the circuit, a question asks to determine the voltage V_x across the dependent current source, with a handwritten answer of -0.2.

Again your given some V_x , which is over here you can first of all see that V_x is nothing, but i_1 times 1 kilo ohms. So, if you find i_1 you find this it is of course, possible to treat this is separate problem and use whatever circuit analysis method you want and find the answer. But, if you already set up the mesh equation and also the point of this assignment is learn mesh analysis, you can solve the mesh analysis equations and find out not only i_1 , but all the mesh currents.

We know that i_1 i_2 i_3 is basically 3 minus 2 1 minus 1 4 minus 2 0 minus 1 3 inverse with units of Millisiemens, this matrix the resistance matrix as units of kilo ohms its inverse will have units of Millisiemens times the source vector which as we saw was half volt minus 2 volts and minus 2 volts. And if you calculate i_1 i_2 i_3 it turns out to be minus 0.2 milli amps minus 1.06 milli amps and minus 1.02 milli amps for our calculation of course, we need only i_1 , so V_x is i_2 times 1 kilo ohms, which is minus 0.2 volts and that is what is given here, so the correct answer for V_x is minus 0.2 volts.

Now, with these solutions; that is, knowing the value of i_1 , i_2 and i_3 you can calculate any variable in the circuit.

(Refer Slide Time: 13:33)

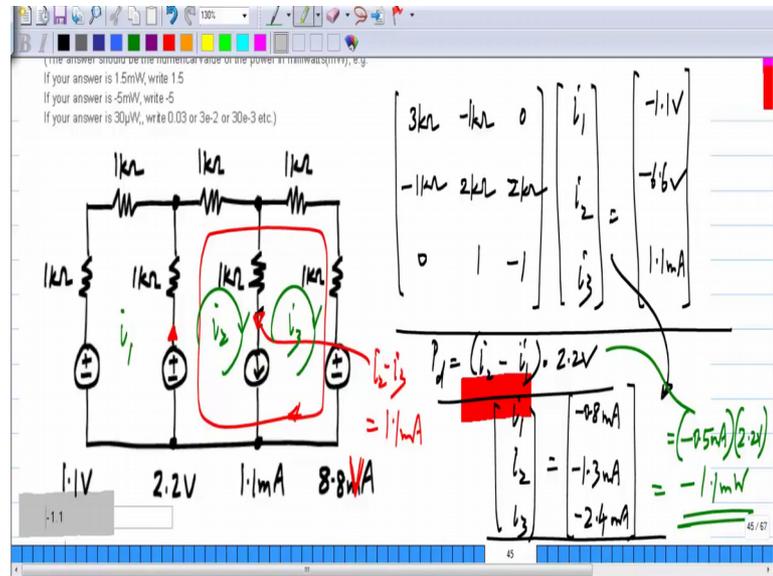

Now, coming to the next problem you have a circuit, you ask for the power delivered by the 2 point volt sources. Now, since the answer require to the power delivered you can again go and do it any way you want, what the whole point of these assignment is to learn mesh analysis, so I am going to use that. Now, in these circuits if you see we have resistors independent voltage sources and an independent current source. So, we have to use this super mesh concept.

So, let say this is i_1 this is i_2 this is i_3 these are three mesh currents, because now there is branch with the, with an the independent current source we have to form a super mesh around it and right the KVL equation around the super mesh. So, first the equation for the regular mesh total resistance in the first mesh, which is 3 kilo ohms resistance common to meshes 1 and 2, which is 1 kilo ohms. So, it appears minus 1 there and the no resistance common to meshes 1 and 3, so 0 over there.

On the right hand side we have the total voltage raise, which is plus 1.1 minus 2.2, which is minus 1.1 volts. And secondly, we have to write the super mesh equation and in the supper mesh equation i_2 is flowing through these two resistors, so the total is 2 kilo ohms and i_3 is flowing through these two resistors in the super mesh, so that is also 2 kilo ohm. And finally, i_1 is flowing through this resistor in the opposite direction to the

direction we use for traversing the super mesh, so the coefficient of i_1 is minus 1 kilo ohm.

In other words, 1 kilo ohm is the resistance common to the super mesh and some other mesh and the total voltage rise in the super mesh is plus 2.2 minus 8.8 volts, so there is the mistake here this should be 8.8 volts. So, we have minus 6.6 volts over there plus 2.2 minus 8.8. When finally, we have to write the relationship between the currents in the super mesh we know that the current in this branch is i_2 minus i_3 in terms of the mesh currents.

So, this current here is i_2 minus i_3 and we know what its value is that is equal to this independent current source, which is 1.1 milli amperes. So, the third equation simply states this fact which is that i_2 minus i_3 equals 1.1 milli amperes, the entries in the, so called in the resistance matrix are both resistances and dimensional constant and the entry in the source vector or both voltages and currents. How do you find the power delivered by this? So, the power delivered by these 2.2 volt sources is 2.2 volts times the current flowing in that direction opposite of the passive sign convention.

The other hand if you take this V and the current flowing in that direction and multiply the two that will be the power dissipated in 2.2 volts. So, now, you can see that this current that is flowing upwards is nothing but, i_2 minus i_1 the current in this branches i_2 minus i_1 flowing upwards. So, the power dissipated is i_2 minus i_1 times the voltage of the voltage source, which is 2.2 volts. Now, to do this we can solve for i_1 , i_2 , i_3 from the mesh analysis set up.

So, solution vector i_1 , i_2 , i_3 turns out to be minus 0.8 milli amperes minus 1.3 milli amperes and minus 2.4 milli amperes. So, i_2 minus i_1 is minus 1.3 minus of minus 0.8, so this term here is minus 0.5 milli amperes, so this is equal to minus 0.5 milli amperes times 2.2 volts, which is really minus 1.1 milli watts. So, it turns out that this 2.2 volt voltage source is actually dissipating power it is dissipating 1.1 milli watt and, because we calculated the power generated it came out as minus 1.1 milli watts and that is the answer shown over there.

(Refer Slide Time: 19:50)

6) In the figure below, 1 point

- I_x is 1mA when I_1 is 2mA and V_2 is -5V
- V_x is 6V when I_1 is 8mA and V_2 is -10V

Determine the power dissipated in the $2k\Omega$ resistor when I_1 is 6mA and V_2 is 15V.

(The answer should be the numerical value of the power in milliwatts (mW), e.g. If your answer is 1.5mW, write 1.5
If your answer is -5mW, write -5
If your answer is 30μW, write 0.03 or 3e-2 or 30e-3 etc.)

Handwritten notes and equations:

$$V_x = 0.5k\Omega(I_x) - (I_1) / 5V = 0$$

$$V_x = \alpha_1 \cdot I_1 + \alpha_2 \cdot V_2$$

$$I_x = \beta_1 \cdot I_1 + \beta_2 \cdot V_2$$

$$I_x = V_x / 2k\Omega \Rightarrow V_x = I_x \cdot 2k\Omega$$

$$2V = \alpha_1 \cdot 2mA + \alpha_2 \cdot (-5V)$$

$$6V = \alpha_1 \cdot 8mA + \alpha_2 \cdot (-10V)$$

$$\alpha_1 = 0.5k\Omega; \alpha_2 = -0.2$$

The next question you are given some circuits, so this m consists of only resistors it means something, which already means and there are some two sources. Now, in this context the network and consisting only of resistors means that whole network is linear with two independent sources i_1 and V_2 . So, this means that any branch variable anywhere in the circuits either with in m or in these will be of the form some proportionality constant α_1 times i_1 plus some other proportionality constant α_2 times V_2 α_1 and α_2 have different dimensions, but that is not relevant the point is this can be expressed this way.

Similarly, you take some other variable, let us say I_x . it will be some β_1 times i_1 plus some other β_2 times V_2 . Because, we have only two independent sources and the rest of the circuit is linear every variable in the circuits either voltage or current is a linear combination of i_1 and V_2 . Now, you are given some conditions I_x is 1 milli amp i_1 is 2 milli amps and V_2 is minus 5 volts and V_x is 6 volts i_1 is 8 milli amps and V_2 is minus 10 volts here first of all we have 4 variables α_1 α_2 β_1 and β_2 , so we have to determine these things.


Now, we also know that I_x equals V_x divided by 2 kilo ohms that is from the definitions here or V_x is I_x times 2 kilo ohms. So, now, in that case we can set up two simultaneous equations that is I convert this also I_x or I convert this also do V_x . So, let me take the first case itself I_x is 1 milli amp, which means that V_x is 1 milli amp times 2 kilo ohms,

which is 2 volts. So, 2 volts equals when i_1 is 2 milli amps that is α_1 times 2 milli amps plus α_2 times V_2 , which is minus 5 volts this correspond to the condition given over there, what it says i_x is 1 milli amp for I know that if I_x is 1 milli amps V_x will be 2 volts.

Because, that 1 milli amp is for 2 kilo ohm resistor and V_x is measured across it and V_x is 6 volts that is 6 equals α_1 times i_1 is 8 milli amps plus α_2 , which is minus 10 volts. So, by solving for these two we can find α_1 and α_2 and if you do that you will get you get α_1 to be 0.5 kilo ohms it has dimensional kilo ohms because it multiplies current to result the voltage and α_2 is minus 0.2 and this is dimension less, because it multiplies voltage to give your voltage.

If you substitute these for the given the values I_2 is 6 milli amps and V_2 is 15 volts you will get this V_x , which is the voltage across the 2 kilo ohm resistor to the half kilo ohms times 6 milliamp minus 0.2 times 15 volts, which is exactly 0. So, it turns that I_2 is 6 milliamps, so V_2 is 15 volts. This, the voltage across this 2 kilo ohms exactly 0 and; obviously, no power is dissipated and 2 kilo ohm resistor. So, that is the answer over there that is 0.

(Refer Slide Time: 24:35)

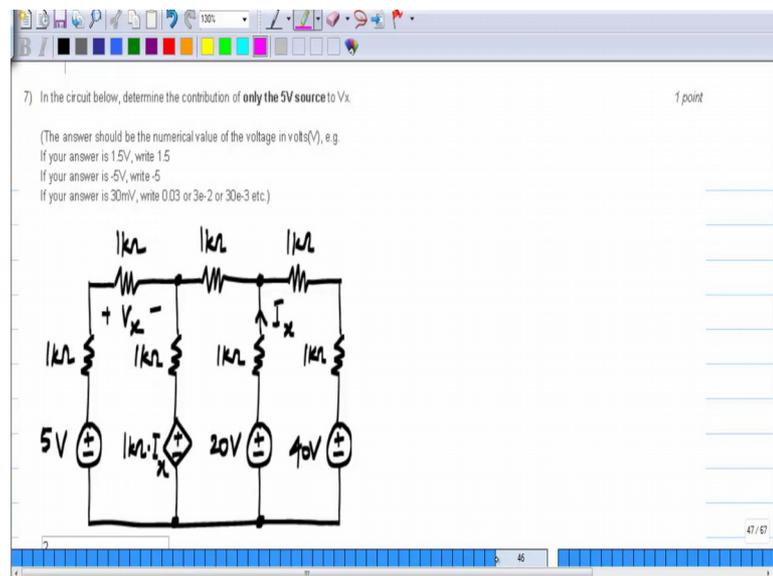

In the next question your ask to find the contribution of on the 5 volts source to be x of course, it can be done and many ways by initially setting this 20 volts and 40 volts sources is 0. Again in the spirit of learning mesh analysis I am going to continued used

mesh analysis. So, in this case we have a circuit with independent voltage sources resistors and in current control voltage source.

Now, if you compare the circuits to the one we saw earlier you see the exactly the same except that the values of these voltage sources are now different. So, this means that basically the resistance matrix will be remain exactly to the same the right hand source vector will be different.

(Refer Slide Time: 25:35)

7) In the circuit below, determine the contribution of **only the 5V source** to V_x .

(The answer should be the numerical value of the voltage in volts (V), e.g. If your answer is 1.5V, write 1.5
If your answer is -5V, write -5
If your answer is 30mV, write 0.03 or 3e-2 or 30e-3 etc.)

Handwritten notes:
 $V_x = I_x \cdot 1k\Omega$
 $V_x = 2V$
 $i_1 = 2mA$
 $i_2 = 5V$
 $i_3 = 2mA$

Resistance Matrix R :

$$\begin{bmatrix} 3k\Omega & -2k\Omega & -1k\Omega \\ -1k\Omega & 4k\Omega & -2k\Omega \\ 0 & -1k\Omega & 3k\Omega \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 5V \\ -20V \\ -20V \end{bmatrix}$$

Inverse Matrix R^{-1} :

$$\begin{bmatrix} \frac{2}{5} & \frac{1}{5} & 0 \\ \frac{1}{25} & \frac{1}{25} & \frac{1}{5} \\ \frac{1}{25} & \frac{2}{25} & \frac{2}{5} \end{bmatrix} \cdot 1mS$$

Final Calculation:


$$\begin{bmatrix} \frac{2}{5} & \frac{1}{5} & 0 \\ \frac{1}{25} & \frac{1}{25} & \frac{1}{5} \\ \frac{1}{25} & \frac{2}{25} & \frac{2}{5} \end{bmatrix} \cdot \begin{bmatrix} 5V \\ -20V \\ -20V \end{bmatrix}$$

So, the resistance matrix it turns out is exactly the same as in the earlier problem, let me show you again, which one that is and this is problem number 3 and this is the resistance matrix. And right hand side we have the voltage rise in the first mesh, which is 5 volts the voltage rise in the second mesh, which is minus 20 volts and the voltage rise in the third mesh which is plus 20 minus 40 volts, so I have again minus 20 volts.

Now, we have to find V_x and also not V_x completely put only the contribution of 5 volts and we know that V_x is i_1 . So, by the way I dint mark the mesh currents i_1 i_2 i_3 are the three mesh currents and V_x is I_2 times 1 kilo ohm. So, if we do this will get i_1 i_2 i_3 to be the inverse of this matrix, which happens to be $\frac{2}{5}$ by $\frac{1}{5}$ 0 by $\frac{1}{25}$ $\frac{1}{25}$ $\frac{1}{5}$ by $\frac{1}{25}$ $\frac{2}{25}$ $\frac{2}{5}$ with units of Millisiemens times the source vector, which is 5 volt minus 20 volts and minus 20 volts.

We are required to find the contribution of only 5 volt source, so we can set these two 0, then you see that i_1 is simply this number here 2 by 5 times 5 volts and times 1 Millisiemens. So, i_1 due to the five volts source alone is 2 milli amps it is the product of this number and that number. So, $V \times$ which is I_1 times 1 kilo ohm is 2 milliamp is to 1 kilo ohm. So, $V \times$ due to the 5 volts source by itself is 2 volts, which is the product of this 2 milli amps and 1 kilo ohm and as you can see that is the right answer.

(Refer Slide Time: 29:01)

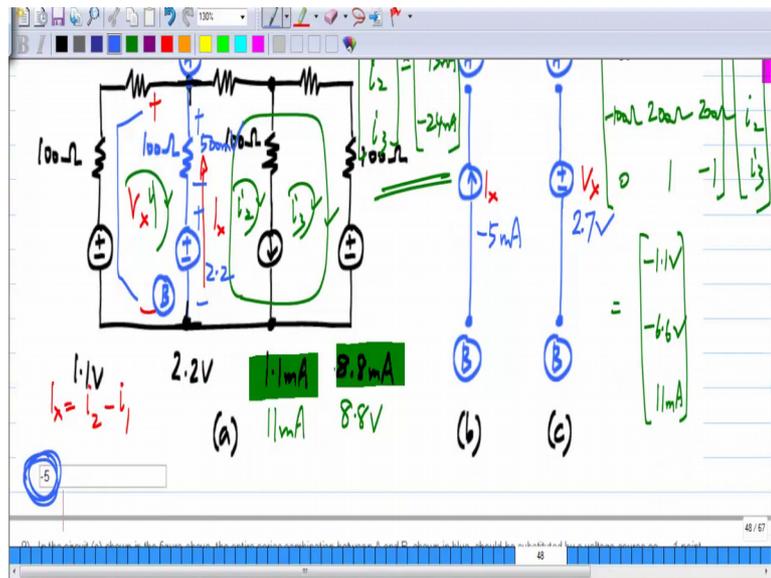

If you go to the next problem you are given some circuit and your asked to replace this entire plans between A and B consist of a resistance and a voltage source and series with current source actually it does not matter what this consists of all you have do is if you have a branch if find the branch current and you have to use the current source whose value equals that current. Now, essentially because this current source with which we have to substitute this flowing from bottom to top we have to find the current flowing that way and let me call that I_x , so current source of value i_x will do the job.

Similarly, when you want substitute with voltage source all you have to do it does not matter again what exactly is in this branch all you have do is find this voltage, let us called V_x then if you use voltage source of value V_x that way it will do the job. Now, again you can do this anywhere you want I will continued used mesh analysis. So, now, in this case we have an independent current source, so we have to use is super mesh surrounding these two meshes that way let me define i_1 i_2 and i_3 .

By the way again there seems to be a mistake here this is 11 milli amperes and this is 8.8 volts these one corrected in the assignment in my copy is not corrected. So, the equation for the first mesh will have the total resistance 300 ohms here resistance common between mesh 1 and 2, which is minus 100 ohms over there and this nothing common three meshes 1 and 3. So, it will be $0 \ i_1 \ i_2$ and i_3 and for the super mesh i_2 is multiplied by these two resistors.

So, that is 200 ohms i_3 is multiplied by these 2 resistors, which is also 200 ohms in total and this one basically it is the resistance common to the super mesh and mesh number 1 that is 100 ohms, so we get minus 100 ohms over there. And finally, if you look at the last equation that is for this current source the current in this branch is i_2 minus i_3 and that has to be equal to 11 milli amperes, so have i_2 minus i_3 equals 11 milli amperes.

The other two entries will be the voltage rise in the first mesh, which is 1.1 volt minus 2.2 volts minus 1.1 volt and the voltage rise in the super mesh, which is plus 2.2 volts minus 8.8 volts, which is minus 6.6 volts. And if you solve for this you will get $i_1 \ i_2$ and i_3 you invert the matrix and you solve for it and it comes out to be minus 8 milli amps minus 13 milli amps and minus 24 milli amps and it makes sense, because I_2 minus i_3 , which is the current flowing down words is 11 milli amps.

Now, in our case we have to find the current I_x and this I_x is nothing but, i_2 minus i_1 , which is minus 13 plus 8, which is minus 5 milli amps, so if you sub suiting this branch shown in blue with current source shown in this direction it has to be sub suited with minus 5 milli amps and that is the answer. Now, the very next question asked for the same branch to be sub suited by a voltage source.

So, we have to find the voltage V_x across these two points we know that the voltage drop across the 100 ohm resistor in this direction is i_1 minus i_2 times 100 ohms and I_1 minus and I_2 is 5 milli amps. So, this is 500 milli volts or half volt and these voltages 2.2, so the total is 2.2 plus 0.5 volts, which is 2.7 volts. So, instead of substituting into the current source of minus 5 milli amps we can also sub suited the voltage source in this polarity of 2.7 volts and that is we have over there, so that takes care of assignment 5.