

Circuit Analysis for Analog Designers
Prof. Shanthi Pavan
Department of Electrical Engineering
Indian Institute of Technology, Madras

Lecture - 05
Tellegen's Theorem and reciprocity in linear resistive networks

People, good evening and welcome to advance electrical networks, this is lecture 3.

(Refer Slide Time: 00:26)

Tellegen's Theorem

- * 2 networks having the same graph
- * $\sum_k v_k \hat{i}_k = \sum_k \hat{v}_k i_k = \sum_k v_k i_k = \sum_k \hat{v}_k \hat{i}_k = 0$

In the last class we looked at Tellegen's theorem and it pertains to two networks having the same graph and is it necessary that the two networks be linear? There is no nothing that says that the networks have to be linear or time invariant. So, the only requirement is that the two networks have the same graph. And what does it say? It says that you know sigma over all the branches $v_k i_k$ is the same as sigma over $k, v_k \hat{i}_k$ must be equal to sigma $v_k i_k$ as which is the same as $v_k \hat{i}_k$ is all equal to 0 and we saw how this comes about right.

$$\sum_k v_k \hat{i}_k = \sum_k \hat{v}_k i_k = \sum_k v_k i_k = \sum_k \hat{v}_k \hat{i}_k = 0$$

(Refer Slide Time: 02:11)

The image shows a man in a blue and white checkered shirt sitting at a desk. Behind him is a large digital whiteboard with a grid pattern. At the top left of the whiteboard is the NPTEL logo. A mathematical equation is written on the whiteboard: $\sum_k \hat{v}_k \hat{i}_k = \sum_k v_k i_k = \sum_k \hat{v}_k i_k = 0$. The equation is partially obscured by green rectangular redaction boxes. The whiteboard also features a toolbar with various drawing and editing tools at the top.

These two are of course, you know immediately understandable and apparent. You may say well you know at any instant of time it seems reasonable that power is conserved right. These on the other hand at first sight seem little puzzling, but we saw a simple network construct that helped us get intuition into why the physical reason why this makes sense right.

All that we did was to put in parallel with every branch of the network, a current which flows in the opposite direction with the value i_k hat and if you now apply power conservation to this network its apparent that you basically get the other two identities. Now, it turns out that Tellegen's theorem is also very useful to prove a whole lot of interesting theorems.

(Refer Slide Time: 03:13)


The slide contains the following content:

- NPTEL Logo** and a software toolbar at the top left.
- Equation:**
$$\sum_k \hat{v}_k \hat{i}_k = \sum_k v_k i_k = \sum_k \hat{v}_k i_k = 0$$
- Text:** Reciprocity: Linear network
* Resistors only (no controlled sources)
- Diagram:** Two circuit diagrams of a linear network N with two ports. The first diagram shows a current source \hat{i}_1 at port 1 (terminals 1 and 1') and a voltage \hat{v}_2 measured across port 2 (terminals 2 and 2'). The second diagram shows a current source \hat{i}_2 at port 2 and a voltage \hat{v}_1 measured across port 1.

The first one that I like to draw your attention to is reciprocity and the idea is the following. So, let us say you have a linear network now ok and we have the same another copy of the linear network, its let us assume its it has two ports 1, 1 prime and 2, 2 prime. This is 1, 1 prime and 2, 2 prime and this is i_1 , this is v_2 and here I inject i_2 hat, and measure the voltage at port 1 is v_1 hat.

Further let us assume that this a linear network which consists of resistors only, in other words there are no controlled sources inside the network. And we apply Tellegen's theorem to both these networks and let us see what happens.

(Refer Slide Time: 05:11)

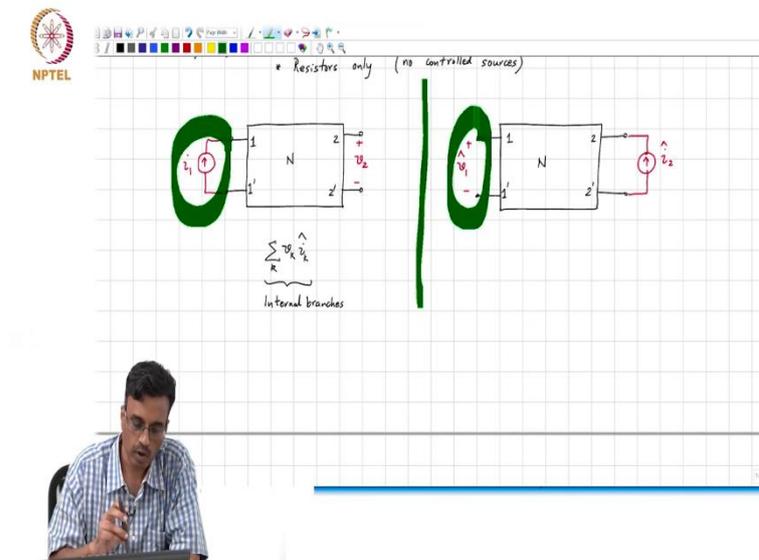

Remember sigma over all branches ok, inside this network N of $\sum_k v_k \hat{i}_k$ which correspond to the branch currents in the; remember the unhatted quantities correspond to the network on the left, the hatted quantities correspond to the network on the right. So, and the k runs over all the branches which are sitting inside the box.

So, if I want to form the product $v_k \hat{i}_k$ for all the; for all the branches in this entire network you have this which corresponds to the internal branches right and what comment can you make about $v_k \hat{i}_k$ as far as the port branches and currents are concerned, what is; we do not know the voltage reforming the product $v_k \hat{i}_k$.

We do not know the voltage across this branch. Right, but we need to find the product of this voltage and this current and what does that happen to be? Well, the current in port 1 of the network on the right is 0. So, therefore, it must follow that the product of $v_1 \hat{i}_1$ is 0.

(Refer Slide Time: 07:07)

The slide shows two circuit diagrams separated by a vertical green line. The left diagram is a network 'N' with port 1 on the left and port 2 on the right. Port 1 has a current i_1 entering. Port 2 has a voltage v_2 across it. The right diagram is the same network 'N' with port 1 on the left and port 2 on the right. Port 1 has a voltage v_1 across it. Port 2 has a current i_2 entering. Below the diagrams, the text reads 'Resistors only (no controlled sources)'. The Tellegen's theorem equation is written as:

$$\text{Tellegen's Theorem} \left\{ \begin{aligned} & -v_2 \hat{i}_2 + \sum_k v_k \hat{i}_k = \sum_k \hat{i}_k R_k \\ & = -v_1 i_1 + \sum_k v_k i_k = \sum_k i_k R_k \end{aligned} \right.$$

Internal branches are indicated by a bracket under the summation terms. To the right of the equations, the relationships $v_k = R_k i_k$ and $v_k = R_k \hat{i}_k$ are noted.

And the only other quantity to consider is $v_2 \hat{i}_2$, ok. Actually, I mean this is our voltage v_2 hat, it must actually be $-\hat{i}_2$ simply because if we assume v_2 to be in that direction, branch current should flow in the opposite direction. So, it is $-v_2 \hat{i}_2$. And this must be equal by Tellegen's theorem, sigma over all internal branches $v_k \hat{i}_k$ correct.

$$= \sum_k \hat{v}_k i_k$$

That is the all-internal branches then, we need to deal with the external the port quantities and, so what is \hat{v}_k ? For the first one it must be $\hat{v}_1 \times -i_1$ ok and what comment can we make about the second port? v_2 hat times the current in port 2 which happens to be? 0 correct. So, this is what Tellegen's theorem throws up.

$$-v_2 \hat{i}_2 + \sum_k v_k \hat{i}_k = -\hat{v}_1 i_1 + \sum_k \hat{v}_k i_k$$

We still have not exploited the fact that the network is linear and that every branch is a resistor right. So, v_k therefore, how is it related to the how is the branch current related to the branch voltage? Right, simply nothing but some R_k times i_k and likewise v_k hat is R_k times i_k hat.

$$v_k = R_k i_k$$

$$\hat{v}_k = R_k \hat{i}_k$$

So, this therefore, means that this part will become sigma sum over all branches inside $i_k \hat{i}_k R_k$ and this will also become sigma over all $i_k \hat{i}_k R_k$. And therefore, what comment can we make about what does this throw up? If you; so, these two quantities evidently are the same. So, these two are therefore, the same and therefore, what do we get?

(Refer Slide Time: 09:57)

NPTEL

Tellegen's Theorem

$$-v_2 \hat{i}_2 + \sum_{\text{Internal branches}} v_k \hat{i}_k = -v_1 \hat{i}_1 + \sum_{\text{Internal branches}} v_k \hat{i}_k$$

$$v_2 \hat{i}_2 = v_1 \hat{i}_1$$

Reciprocity

$$\frac{v_2}{\hat{i}_1} = \frac{v_1}{\hat{i}_2}$$

$V_2(j\omega) = \frac{\hat{V}_1(j\omega)}{\hat{I}_2(j\omega)}$

$v_2 \hat{i}_2 = v_1 \hat{i}_1$ which is equivalent to saying that v_2 by \hat{i}_1 is the same as v_1 by \hat{i}_2 .

$$v_2 \hat{i}_2 = v_1 \hat{i}_1$$

$$\frac{v_2}{\hat{i}_1} = \frac{v_1}{\hat{i}_2}$$

So, this is the reciprocity right because we now only did this for network with resistors. It follows I mean it is you go through the same proof and show that it is easy to see that.

(Refer Slide Time: 11:24)

If you are if you have impedances ok, V_2 of $j\omega$ by I_1 of $j\omega$ is V_1 hat of $j\omega$ divided by I_2 hat of $j\omega$. The proof is exactly the same. Make sense? Yes.

$$\frac{V_2(j\omega)}{I_1(j\omega)} = \frac{\hat{V}_1(j\omega)}{\hat{I}_2(j\omega)}$$

So, in other words the transfer function I mean the what do you seen in the past is basically you know the one way to say it is that well if you have a linear network with only resistors or impedances then you can interchange the location of the excitation and the response and you get the same transfer function.

One thing that I would like to point out is that if you de energize all the sources ok, so, in other words this is not around and neither is this what comment can you make about the network about both the networks? So, if I remove i_1 on the left and i_2 hat on the right, if I look at the two pictures what are they? It is exactly the same.

So, please bear that in mind when you apply a reciprocity right. If the graphs of the network are not the same then you know you will not get, I mean this condition will not be satisfied. So, we have seen current input and a voltage output, it turns out that you know you can work this out at home.

(Refer Slide Time: 13:11)

The whiteboard content includes:

- Left circuit: A voltage source v_1 connected to a network N with terminals 1, 2, 1', and 2'. The output voltage is v_2 .
- Right circuit: A voltage source \hat{v}_2 connected to the same network N . The input voltage is \hat{v}_1 .
- Claim: $\frac{v_2}{v_1} = \frac{\hat{v}_2}{\hat{v}_1}$ (marked with a red 'X')
- Equivalent circuit 1: A voltage source v_1 in series with resistor R_1 , connected to a resistor R_2 . The output voltage is v_2 . The current is labeled $i_1 + i_2$.
- Equivalent circuit 2: A voltage source \hat{v}_1 in series with resistor R_1 , connected to a resistor R_2 and a voltage source \hat{v}_2 . The output voltage is \hat{v}_2 .

But the same thing happens when you have or rather, I would say a similar thing happens when you have voltage input. So, this is v_1 and this is v_2 and what should I do? Does somebody know what I should do? Ok, so well I have the answer I get is ok how about exiting this and the sorry this is \hat{v}_2 and this is \hat{v}_1 , the claim is that v_2 by v_1 is \hat{v}_2 by \hat{v}_1 is the same as what? \hat{v}_1 by \hat{v}_2 . This is the claim right and I see all of you nodding your heads you know, it is correct?

Exactly right. So, this is tempting to kind of say, but this is actually not correct alright, remember that the graphs of the network when you de energize the sources must be the same. So, when you de energize the sources what do you get on the left side which port is shorted?


Port 1 is shorted in the on the network on the right port 2 is shorted. So, you do not have the same graph on both the sides and therefore, you know the this is definitely not correct. And if you want a simple analogy a simple counter example here it is this is R_1 . I still see people kind of incredulously looking at the result and saying how can that be. So, this is v_1 ok.

So, what is the output voltage? R_2 by R_1 plus R_2 times v_1 ok.

$$\frac{R_2}{R_1 + R_2} V_1$$

Now, I take the same network as you guys suggested. I will apply v_2 hat here and what is v_1 hat? v_1 hat is? v_2 ok. So, clearly you can see that the transfer functions are not the same right and the reason is that you know the graph of the network is ok. So, now that this is wrong what is right is what we are do.

(Refer Slide Time: 17:23)

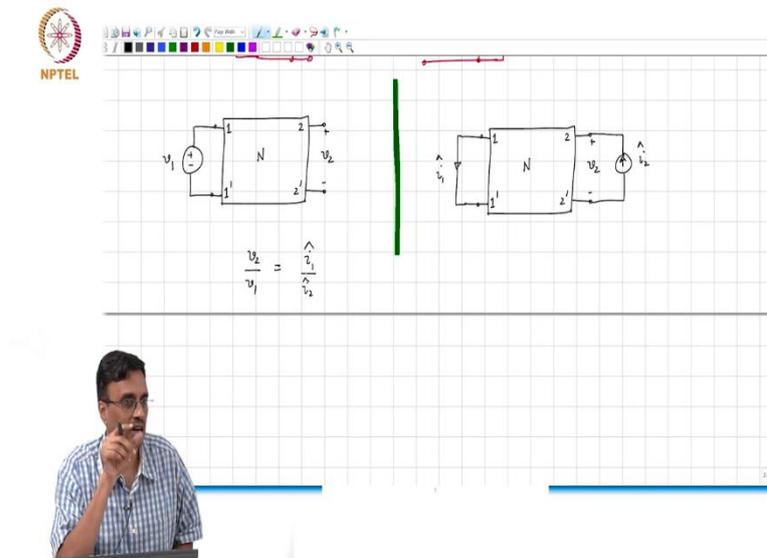

So, what do you think the correct answer is? Short ports. So, the correct expression of reciprocity is basically to look at i_1 hat and you apply what should I apply on this side? Remember v_1 and v_2 the input is a voltage the output is a voltage. Correct. So, what you have to apply is a current i_2 hat and measure the current i_1 hat ok. And it so turns out I mean you can simply go through the same arguments that we went through to prove the other result. I leave that for you as home work and convince yourselves that v_2 by v_1 equals? i_1 hat by i_2 hat ok.

$$\frac{v_2}{v_1} = \frac{\hat{i}_1}{\hat{i}_2}$$

The voltage transfer function in the network on the left is the same as the current transfer function on the network on the right and whenever you do this you always will be in good stand if you run the sanity check namely when you de energize the sources the graphs must be the must be the same. No, the I we said already that N only consists of resistors right.

An impedance right, but impedance is not a source right. It reciprocity applies to a linear network where all the branches currents can be expressed linearly as a function of with the

branch voltages right. So, if you look at see the comment was does it hold for any linear network, it holds for all network. The key point in the argument is, remember, Tellegen's theorem is valid for any network, it does not you know need linearity right.

What is allowing us to basically cancel out all the powers you know the pseudo powers kind of thing dissipated in the branch internal branches. We are able to do that because we are able to express the branch voltage as some R_k times i_k right or in general if there are impedances the branch you know v_k of j omega is some z_k of j omega times i_k of j omega.

As long as that is satisfied you will say you know reciprocity holds. Now one you know practical case where this is automatically satisfied is when you have a linear network which is also passive right when you have only R , L and C in them right which are the commonly known you know the passive elements that we use and it is automatically satisfied.

And you know there is a general misconception that it is only applicable to passive networks right, but that is not the case because for instance if you know I somehow manage to create an impedance which was negative right all that these relationships saying is that v_k is R_k times i_k , the sign of the R could be negative right.

If the resistance is negative, it means that the network is actually active because the resistor is actually pushing out power rather than dissipating it, but that does not affect reciprocity at all, right because these products will cancel out and you still end up with you still end up with the transfer functions being identical.

Control sources is a you know we have still not as far as we are concerned at this point there can be no controlled sources inside the network. Only two terminal linear two terminal elements whose branch currents and branch voltages are linearly related to each other, is that clear.