

Video course on electronics
Prof. D.C. Dube
Department of Physics
Indian Institute of Technology, Delhi

Module No.# 02
Transistors
Lecture No. # 6
Biassing Of Transistors

(Refer Slide Time: 00:39)

The image shows a whiteboard with handwritten mathematical equations. The equations are as follows:

$$I_B R_B + V_{BE} + I_E R_E = V_{CC} .$$
$$\beta = I_C / I_B , I_E \approx I_C .$$
$$\frac{I_C}{\beta} R_B + I_E R_E = V_{CC} - V_{BE}$$
$$I_C = \frac{V_{CC} - V_{BE}}{R_E + R_B / \beta}$$


∴ $R_E \gg R_B / \beta$

$$I_C = \frac{V_{CC} - V_{BE}}{R_E} , I_C \neq f(\beta)$$

In the bottom left corner of the whiteboard, there is a small circular logo with the text "NPTEL" below it.

We will continue our discussion on biasing of transistors; we were talking about the self bias, in which we have shown that the collector current was independent of the changes in beta. And I said earlier that a circuit, which shows a stability against one kind of variation will take care of variations due to other reason; that means the cause of variation is material. This circuit is used as a voltage divider also.

(Refer Slide Time: 01:11)

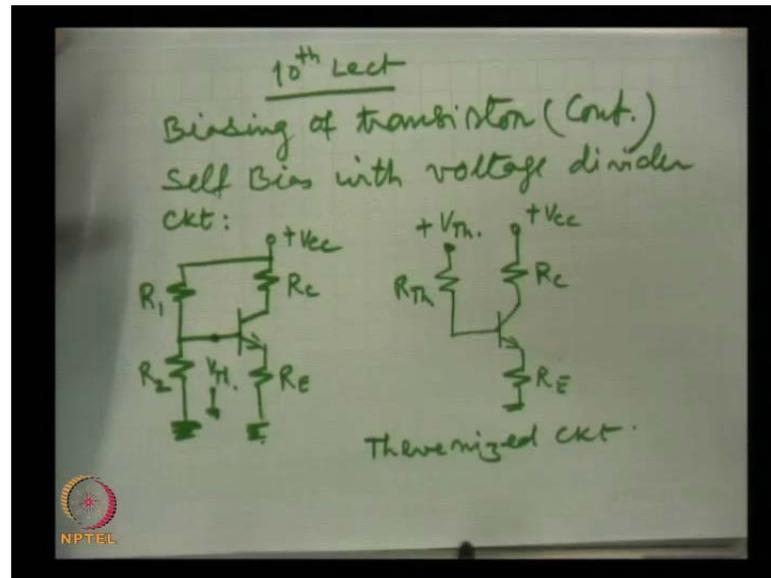


So, self bias with voltage divider circuit. This has certain advantages and those advantages also I will point out, but let us first see, what is this circuit?

(No audio from 01:30 to 02:10)

Here, this is the voltage divider circuit in fact, this is the one self bias, which is very widely used. This has certain advantages, which we will point out. Now, this circuit can be thevenized, the single resistance R_E has been changed with, it has been replaced by two resistances R_1 or R_2 . So, this can thevenized; and thevenized equivalent circuit is this.

This is V_{cc} , R_C , R_E , and this is thevenised voltage, and this is thevenised resistance R_{Th} . So, this is thevenised circuit, which is equivalent of this original circuit. This is actually the design is taking this, but for analysis purposes, we thevenized this; we apply thevenised theorem, and we get the value of the thevenised voltage and thevenised resistance. Now, thevenised voltage is what is the voltage, which is observed between this point and the ground, this is thevenised voltage V_{Th} . and if we complete this circuit here this is V_{cc} .

(Refer Slide Time: 04:08)

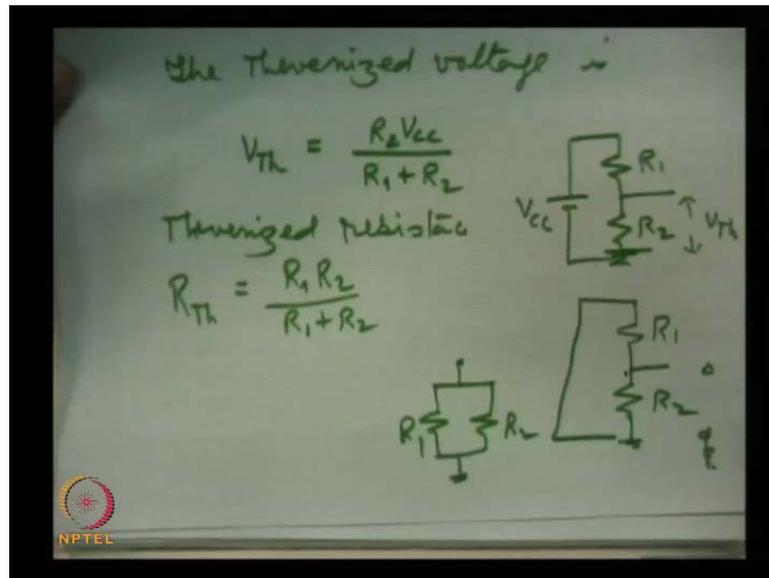

And if we complete this circuit here, this is V_{cc} , then we know that the thevenized voltage will be V_{Th} , this is the current V_{cc} by R_1 , R_2 . Here, that means we are discussing this circuit. Here this is thevenised voltage V_{Th} and this is R_1 , R_2 and this is the battery V_{cc} . So, obviously the current is through the battery V_{cc} by the total resistance and what will be the voltage develop across this, this is the current into R_2 . So, this is the thevenized voltage which we can calculate, and the Thevenized resistance, this **thevenized resistance** for finding the resistance between these two points. The Thevenin's theorem as the must have studied that to calculate the equivalent resistance, we have to ground the dc voltage source.

So, this is grounded, so our circuit becomes this. This becomes the circuit R_1 and R_2 , so as far as this point in ground is concerned, these two resistance are in parallel. This is grounded, it this is grounded so this is like this. R_1 and R_2 they are in parallel so, R_{Th} is equal to R_1 , R_2 by R_1 plus R_2 . So, these are the Thevenized voltage and Thevenized resistance is in the circuit

(Refer Slide Time: 06:59)

$$I_C = \left(\frac{V_{TH} - 0.7V}{R_E + R_{TH}/\beta} \right) \quad V_{BE} = 0.7V$$

$$R_E \gg R_{TH}/\beta$$

Two main advantages

1. $R_{TH} < R_1 \approx R_2$

2. $(R_1 + R_2) > R_1 \approx R_2$
Draw less power.


NPTel

And then that final equation which we wrote for which showed the high stability, that can be the voltage because earlier this terminal was connected to V_{CC} so, that V_{CC} is to be replaced by V_{TH} . So, this is V_{TH} and this is V_{BE} which for silicon transistor 0.7 volts, 0.7 volts divided by R_E plus V_{TH} by R_{TH} Thevenized resistance by beta. This is the expression. And now, so this is the final expression and by making R_E greater than R_{TH} by beta, we can make the collector current independent of the variation. Independent of beta that mean it is independent of the variation of beta and this will be highly stable.

I said that in self bias, voltage divider circuit is widely used and it has advantages. I give, I talk about two main advantages, two main advantages of this voltage divider circuit in compared with the single resistance or B circuit. And these advantages are that this condition R_E resistance should be large, quiet large in comparison to this. This condition is better than satisfied by Thevenin's circuit, Thevenized circuit. We can see here that when two resistance are in parallel, then the effective resistance is the smaller than either. That is the rule of parallel combination if for example, this is 100 ohm this is 50 ohm then the combination will be less than even the smaller resistance. So R_{TH} thevenized equivalent resistance is less than R_1 or R_2 , and hence when this is low then this condition can be better satisfied.


And so, this amounts to better stability and second point which is important, when we are sourcing our circuit by a battery because the battery will see that the two resistance in series and hence the resistance output resistance, output resistance seeing by the battery is higher. R_1 plus R_2 is certainly having higher magnitude, then R_1 or R_2 individually. So, this is that means it will draw less power so the battery life. This is the important in the case when our circuit is powered by a battery, so the battery life will be higher in this case. So, these are the two main advantages for the circuit.

(Refer Slide Time: 11:16)

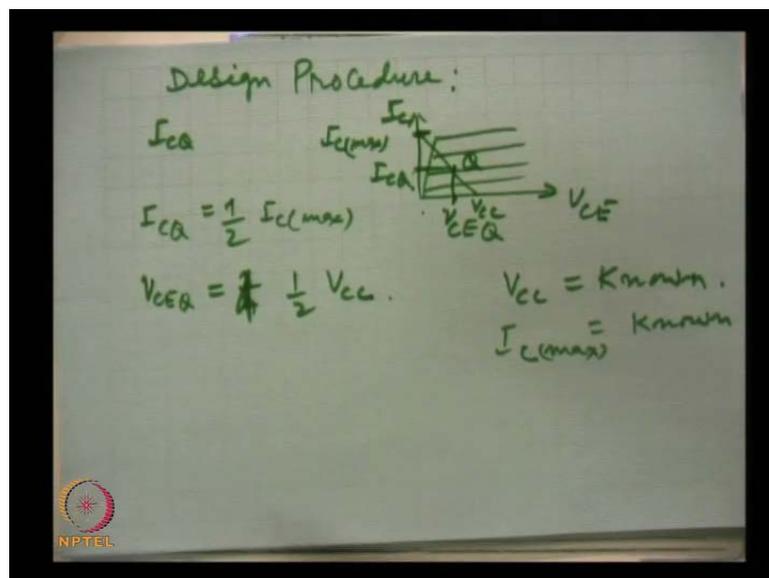


Now, I can repeat the design procedure. Design procedure, you see here if the characteristics are available then we choose the operating point near the middle of the active region, and we already know the value of I_{CQ} . That means the quiescent current, collector current and voltage drop V_{CEQ} can be rear. If these characteristics are not available, as is the often case then it is safe because the manufacture described the values of the $I_{C(max)}$. So, it is safe to take I_{CQ} to be equal to half of this $I_{C(max)}$. So, this point is known and V_{CEQ} can be taken as half of V_{CC} half sorry So, V_{CEQ} is known, I_{CQ} is known and we can used certain, whatever we already study that knowledge that V_{CC} known and $I_{C(max)}$ this is also known, then we can get the value of R_C .

(Refer Slide Time: 13:42)

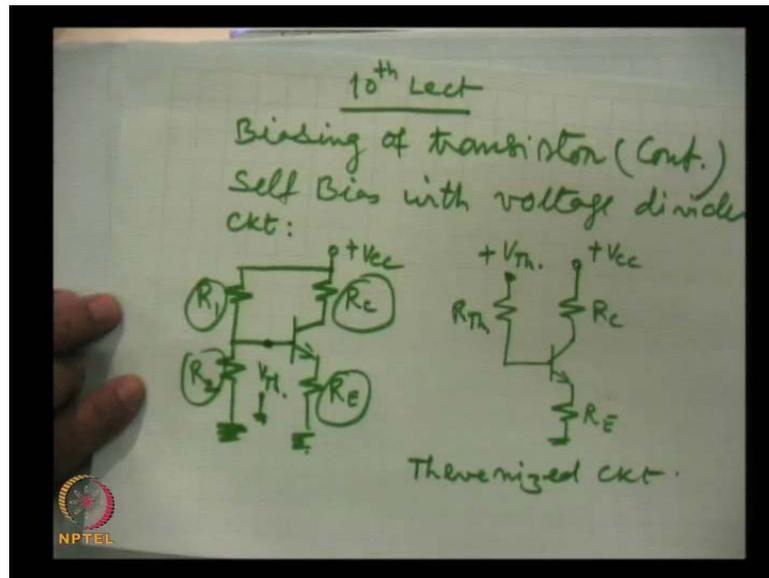

We have to find out the value of R_c , R_1 , R_2 and R_E in the circuit and that is the total design we can assemble the circuit easily.


(Refer Slide Time: 13:59)

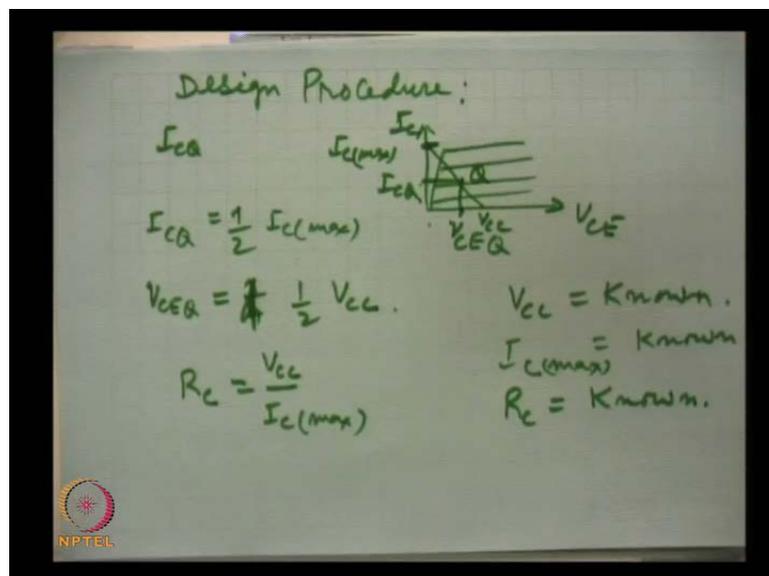

So, R_c can be found out from V_{CC} by $I_{C \max}$. So, now R_c is also known and we remember that if we substitute, if we use the Kirchhoff's voltage law we applied this to the collector circuit, then we get this equation summation of the voltage is $V_{CC} - V_{CE}$. Here I_C is flowing so there is the voltage drop here, this is plus minus V_{CE} and this is


R E through which current I E is flowing and I E and I C are same, so same is almost flowing.

(Refer Slide Time: 15:00)

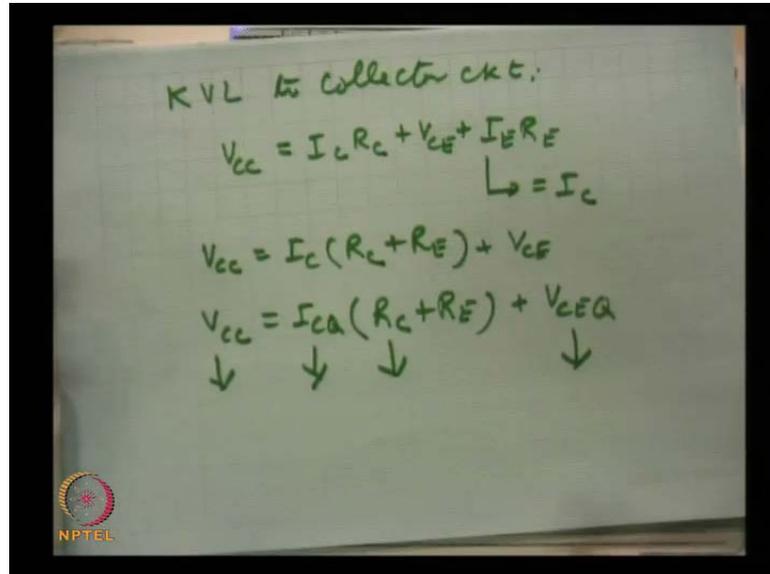

And so, this is equal to I C, R C plus V CE plus I E, R E, but this is equal to, almost equal to IC. So, this equation then becomes V cc, I c and R c plus R E and plus V CE. Now V CE is V CEQ, I c is I CQ so V cc is I CQ, R C, R E plus V CEQ. This is known **this is known this is known this is known**, so except R E all other parameters are known, so we can find out R E.

(Refer Slide Time: 16:07)

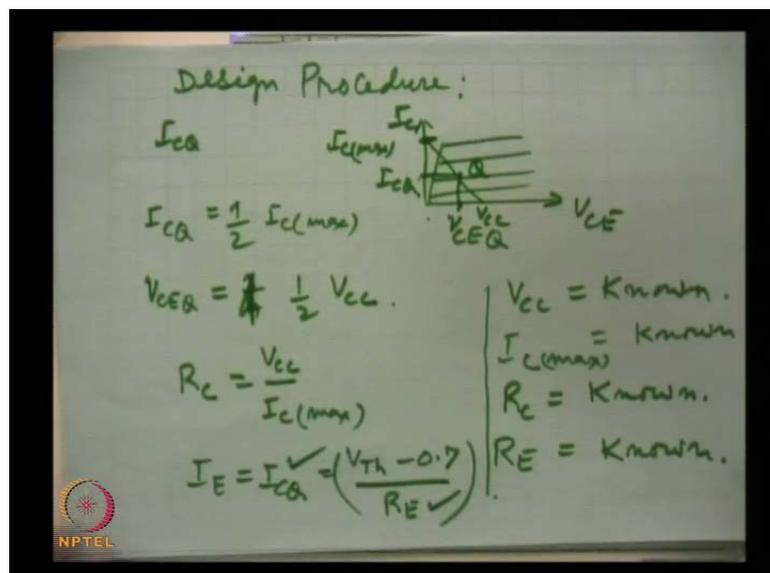

So, in this series R_E is also now known. We have calculated its value, so the R_C is known, R_E is known and the two resistances have to be calculated, and for that we make use of this I_E which is same as I_{CQ} and this is equal to V_{Th} minus V_{BE} by R_E . This is the expression which we have talked about earlier. Now, here this is known **this is known**, so we can calculate the value of V_{Th} .

(Refer Slide Time: 17:08)

Handwritten notes on a grid background:

$$V_{Th} = \text{Known.}$$
$$V_{Th} = \left(\frac{R_2}{R_1 + R_2} \right) \cdot V_{CC}$$
$$R_1 = 3, 10, 1K, 20.$$


Stability factor: 10

NPTEL logo is visible in the bottom left corner of the slide.

V_{Th} is now known, its magnitude is known. Once we know this then V_{Th} is equal to, I have just written the expression is equal to R_2 , R_1 plus R_2 into V_{CC} . So, this is known this is known. Now, one thing one practice is very common in the design of the electronic circuit that we can assume one of the values R_1 for example, we can assume as a 3k, 6k, 10k or 20k and other can be calculated. This is one way, otherwise if we do not want to use our judgment, we can calculate by using the stability factor. Stability factor for a good circuit may be assumed, and say ten and this will give one relationship of a R_1 and R_2 . So, we will have two relation one is here and other will come from stability factor, and by using these two expression, that two the value of R_1 in R_2 can be calculated independent and this way the design is complete, all the parameter of the circuit are known.

So, this was about the self bias and in spite of the fact that this voltage divider arrangement of the self bias makes use one additional resistance, but these two advantage are significant, hence this is most widely used circuit.

(Refer Slide Time: 19:25)

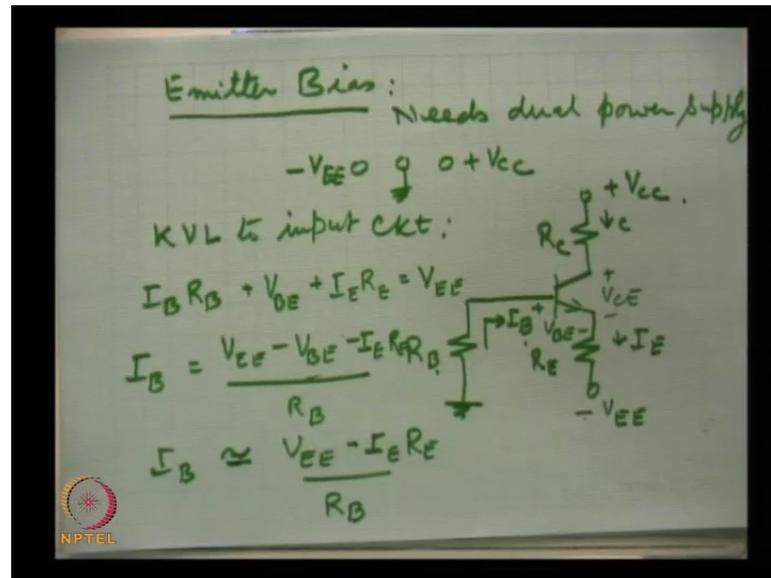

And now, we move to the another biasing scheme and that is Emitter bias **Emitter bias**. As I said in the beginning emitter bias shows stability as high as the self bias circuit but it makes use of dual power supply **needs dual power supply**. And I have explained the meaning of dual power supply and that is two voltages with respect to ground, one is plus V_{CC} other is minus V_{EE} . This power supply is needed to implement Emitter bias and then circuit is simple, and actually this is very popular biasing scheme. Operation amplifier, we will go in details later, is a one of the most important development in electronic.

Today, it is hard to find any circuit analog or digital which does not make use of operational amplifier. So, operational amplifiers are very widely used and operational amplifiers usually make use of this biasing scheme, because it is very simple and stability is as good as the self biasing case. Now the circuit is this R_C , R_E and this is connected to this point, minus V_{EE} and this is connected from here plus V_{CC} and then this is R_B . So, this voltage is usual is V_{CE} and collector current flows here and here is the emitter current and from here flows what is I_B .

This is the circuit and we can show here that how stability will be achieved. Let us apply Kirchhoff voltage law to the input circuit, and that will give $I_B R_B$. This voltage is V_{BE} , so plus V_{BE} and then the drop here, this voltage drop, so plus $I_E R_E$ and this is equal to this voltage, V_{EE} . This is the minus signs, it will come minus V_{EE} , we have

take on this side. And from this we can write I_E , I_B the base current is equal to V_{EE} magnitude, V_{BE} and minus $I_E R_E$ divided by R_B . This voltage is very small in comparison to this voltage, these two voltages may be equal which are normally used like that but, there is a not necessary condition. These two voltages differ also, one may be 12 volts other can be 9 so but, normally as I said that equal magnitude of V_{CC} and V_{EE} are used. Now, from here if the neglect this voltage which is small then I_B becomes equal to, almost equal to V_{EE} minus $I_E R_E$ by R_B .

(Refer Slide Time: 24:37)

$$I_E \approx I_C$$

$$\downarrow I_B = \frac{V_{EE} - I_C R_E}{R_B}$$

Using $I_B = \frac{I_C}{\beta}$ and $V_{BE} = 0.7V$

$$I_C = \frac{V_{EE} - 0.7}{R_E + \frac{R_B}{\beta}}$$

$$R_E \gg \frac{R_B}{\beta}, \quad R_E = \frac{20}{\beta} \cdot R_B$$


$$I_C \approx \frac{V_{EE} - 0.7}{R_E}$$

Now, for any reason I_E is almost equal to I_C and this shows, this is the equation which shows the stability that if this rises current, collector current too rises, this parameter will require higher magnitude and this term will fall. As a result I_B will fall and this fall in I_B will take care of the rise in the rise of the current, because again the output characteristics if you look if I_V falls, the corresponding I_C also falls. So, this is that stability and using I_B equal to I_C by beta and V_{BE} equal to 0.7 volts. This I_C can be written as $\left(\frac{V_{EE} - 0.7}{R_E}\right)$ and if we design the circuit such that this R_E is large comparison to R_B beta by β . By this very large we mean for example, R_E taken twenty times of this factor. This is good enough, if this condition is met than this I_C will be very closely equal to this.

We can drop this term and this shows is stability achieved through any variation in the value of beta because final current, the collector current is the irrespective of this value


beta. So, this shows that it is highly stable circuit, design the simple, number of the resistance used is smaller and high stability. So, this is very widely used by (()) scheme for bjt circuit. Now, the only point is that it needs dual power supply, so which is off course easily available, and so when dual power supply is the available we can use this circuit.

(Refer Slide Time: 27:57)

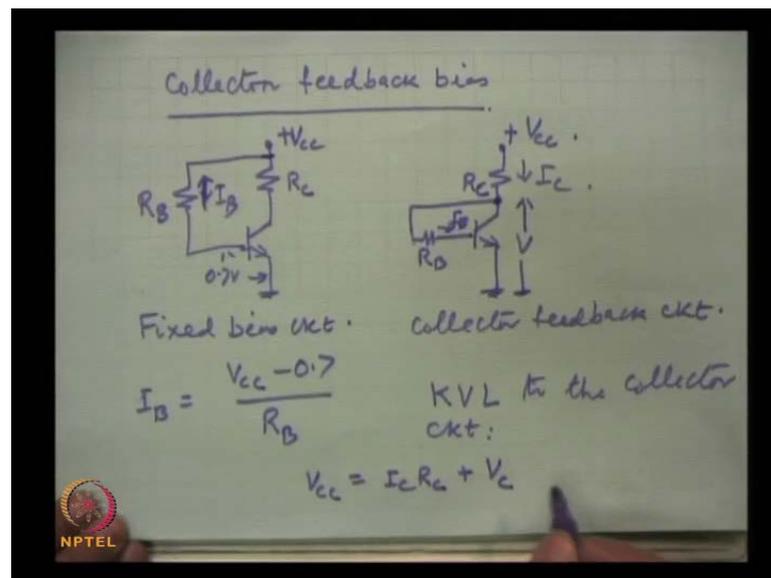

Then the last scheme is collector feedback bias. Collector feedback bias, you see we earlier had this circuit, this was fixed bias circuit. We make a small modification that the terminal is not return to battery, but we can connect here then the circuit becomes this, R B, R C and V CC. This is the collector feedback circuit **collector feed back circuit** it is a small change, just we have moved this point to the other part of the resistance R c and this provides a stability to the circuit, why? Because here the I B, this was simply I, B was simply V CC divided by R B, this voltage is 0.7 volts and this is all fixed. So, this is fixed bias and it is never used with bipolar transistor. This is here, this voltage between this terminal and ground that will control the current I B and this is variable, we can see, we apply the Kirchhoff's voltage law to the collector circuit **to the collector circuit** then we simply get this is I C here so, V CC summation of voltages is equal to I C, R C plus V C.

(Refer Slide Time: 31:40)

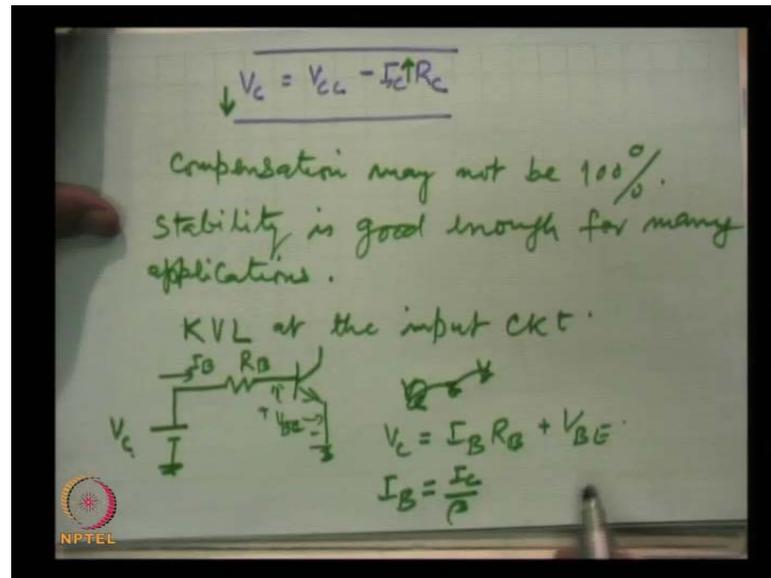

Or we can write that V_c is equal to from this equation. V_c is equal to V_{CC} minus $I_c R_c$. Now, this is the equation which can explain that how stability will be achieved by the collector feedback and look at here, for any reason if I_c rises. So, this term will fall and V_c will go down and this V_c in this circuit will send smaller current, base current, and that will take care of the rise in collector current. It will check the rise in the collector current and this way the stability will be achieved. Now, so this voltage compensates for the rising current and this compensation may not be 100 percent. And that is the reason it was said, that it is much better circuit as compare to the fixed bias.

Fixed bias is never used, this is much better circuit but the stability is good enough for many applications. And this is widely circuit because very simple to design, makes use of fewer resistance, just two resistance is and in the case of the voltage divider circuit there were four resistor required, so the number is reduced to half. When we talk of a system in which several stages of the circuits are there, then the reduction of the resistance is significant to reduce the cost of the circuit, so that is very important point. Now, if very high stability is not the requirement which is true for many application then the collector feedback bias can be used to achieve the stability and we can talk little bit more about the design procedures.

We applied the KVL, the Kirchhoff's voltage law at the input circuit which gives, I will draw the circuit this is the circuit I B. And when we apply the Kirchhoff's summation of

voltages, this voltage is plus, minus V_{BE} . So, then we will get V_C is voltage, V_C equal to I_B into R_B , V_C is equal to I_B into R_B plus V_{BE} and using the relation I_B is equal to I_C by beta we get from here V_C is equal to I_C by beta R_B plus V_{BE}

(Refer Slide Time: 36:26)

$$V_c = V_{cc} - I_c R_c \quad \text{--- (X)}$$

$$V_c = \frac{I_c}{\beta} \cdot R_B + V_{BE} \quad \text{--- (Y)}$$

From Eqs (X) and (Y),

$$I_c = \frac{V_{cc} - V_{BE}}{R_c + R_B/\beta}$$

$$R_c \gg R_B/\beta$$

$$I_c = \frac{V_{cc} - V_{BE}}{R_c}$$

Earlier, this is one equation let us call it y and earlier we obtain the equation V_c equal to V_{cc} minus $I_c R_c$, let us call this X and we can eliminate this V_c because V_c is not known, its unknown quantity. So, this is to be eliminated and we eliminate from here we get from equations x and y, we get I_c equal to V_{CC} minus V_{BE} , R_C plus. So, if we can take care of this condition R_c to be high, compare to R_B by beta. Then this will shows high stability, this term can be dropped may be dropped and I_c will become equal to $V_{CC} - V_{BE}$ divided by R_C . And beta is very high, beta is 100, 200 easily, so this condition is very easy to fulfill. And so, this way we have made the collector current totally independent of the variation of beta and hence a stable circuit. As I said that this shows the stability the design is very simple, makes use of fewer resistance and hence it is widely used.

(Refer Slide Time: 39:12)


Simple design procedure:

$$I_{c(max)} = \frac{V_{cc}}{R_c}$$
$$I_c = \frac{1}{2} I_{c(max)} = \frac{V_{cc}}{2 R_c} \quad \text{--- (X-1)}$$
$$I_c = \frac{V_{cc}}{R_c + R_B / \beta} \quad \text{--- (X-2)}$$
$$\frac{V_{cc}}{2 R_c} = \frac{V_{cc}}{R_c + R_B / \beta}$$

By noting Eqn. (X-1) and (X-2)


We can go for simple design procedure for this and we arrive at a very simple relation, simple design procedure. We know from the load line or from the maximum current I_C , this equal to V_{CC} by R_c and this either form the graph we can take, from the where the load line cuts the y axis or we can used this procedure, which is quiet safe to take a half of I_C max, given by the manufacture in the manual. So, this will be equal to V_{CC} by just we substitute here I_C max, so this is $2 R_c$. This is one equation, let us called X 1 and the equation which we have talked here, this equation that is if we neglect this is the small voltage then the equations becomes I_c is V_{CC} by R_c plus R_B by beta. Let us called X 2, then from this equation, we can simply substitute for I_c this values, so this will be V_{CC} , $2 R_c$ equal V_{CC} , R_c plus R_B by beta. This is equating, we have obtain by equating, equation X 1 and X 2.

(Refer Slide Time: 42:02)

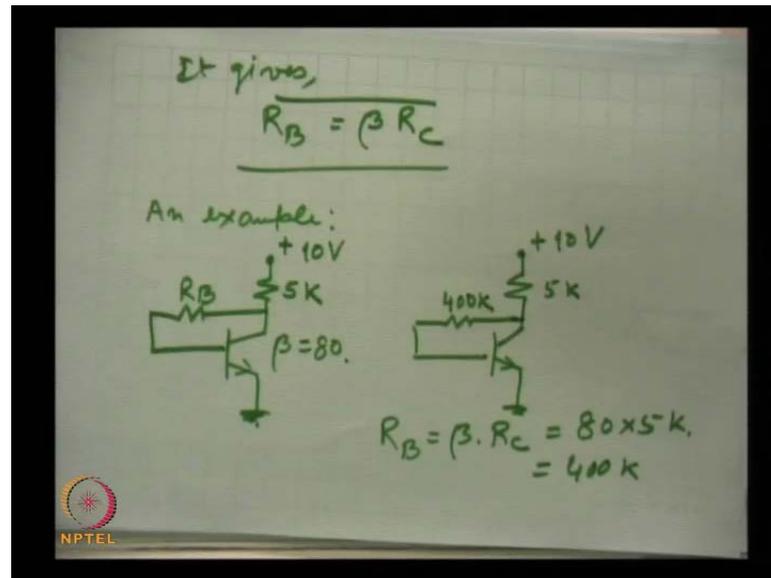

And here this goes and we simply get a relationship that it gives R_B equal to βR_C . This is the simple thumb rule for the calculation of the value of R_B , only there are two resistance in the R_C in R_B and one is known from that maximum current relationship, other is known from here. So, the design of this collector feedback circuit is also very simple. I just take as an example that if this is the circuit, if the β of the transistors comes out to be suppose 80 then we can very easily find out the value of this resistance R_B and so, the circuit will be, this is 5 kilo ohms and this is R_B from this relation R_B is equal to βR_C and this is 80 into 5K so, 400K. So, this resistance say, 400 K so this way, this will give the midpoint operation for the collector feedback bias because this condition

(Refer Slide Time: 44:33)

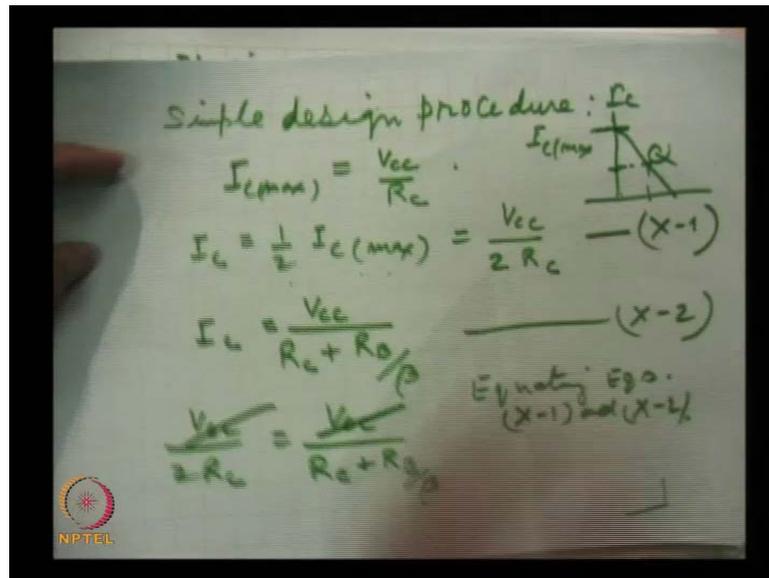

We have used I_C is equal to half I_C max this is for midpoint, because here this is I_C max point and the half of is somewhere in middle. So, we are talking about the Q point in the somewhere in the middle of the active region. So, this is very simple and as I said very widely used, if extremely high stability is not required. So, that finishes this unit two on transistors and the biasing circuit design, circuit thy stability and the design of the biasing circuits. I summaries some of the futures we started with the transistors, the n p n and p n p, for normal operation n p n and p n p work the same way, there is no preference. But as from the discussion you must have gathered that in n p n electron, movement from emitter to collector is that takes the whole working of the transistor and transistor action.

So, and in the p n p the role is taken by the whole electron mobility is higher as compare to whole mobility. So, n p n transistor will perform satisfactorily, will continue perform satisfactorily up to higher frequency ranges. And then we discuss the design of the transistor that the emitter region is most heavily doped, this region is lightest doped and collector is moderately doped. And then from wear we have come to conclusion of these ranges, this we discusses even in terms of what we call, what makes efficient transistors that emitter efficiency, collector efficiency and so on. And base transport factor we discusses and we come out with the same conclusion.

The important thing was, and in that the transistor can be biased such that both junctions can be forward biased, that means we are in the saturation region of the characteristics, and in saturation region the output current and input current both currents are high, but they are independent which is against the requirement for an amplifier. And we can make both transistors reverse biased that is the case again, we are the two currents are false in their emitter circuit and collector circuit, but the two currents are independent. Even if we switch off the emitter current, the reverse saturation current in the collector circuit continues to flow and that is not what we required in an amplifier circuit. So, these two states are widely used, and when we used the transistor as a switch that means in digital electronics.

Here the transistor, we are using as an amplifier. So, the requirement is which is very fundamental that the emitter junction has to be forward biased; the collector junction has to be reverse biased, whether now the transistors can be used in three different configurations: the common base, common emitter and common collector. Common base circuit is fundamental and is very useful when we talk about the theory of transistors. Transistor action was explained through the common base circuit, and what is the transistor action that and from where the name transistor came?

Transistor; (trans resistor), that we transfer the almost the same amount I_E to the collector. So, from emitter resistance is forward biased and the resistance is few times of ohms, to a high resistance circuit, collector circuit which has resistance of the order of several hundred to few thousand ohms. And this transfer is not possible by simple arrangement of resistances and capacitors, this is possible through an active device which is transistors, and this is known as transistor action. So, transistor action is transferring a certain amount of current from low impedance circuit to high impedance circuit and here, so, this is the active region of the characteristics. There we have seen that the collector current totally depends on the input current which is I_B in a common emitter circuit. And then we talked about the three circuits, we will be taking in the next unit. Three amplifier, common base, common emitter and common collector, but let me mention here that common base is rarely used in practice.

The reason is very low input impedance, if a battery is connected then low impedance means, it will draw high current from the battery, so battery life will be extremely poor. There are other reasons; this is no current gain, α is the current gain in common base

circuit and alpha is actually less than one. The output current versus input current, so alpha is I_c divided by I_E and I_C is always less than I_E , but close to that. So, alpha is the current gain which is close to one, but less than one hence there is no current gain, but beta which is the current gain in common emitter circuit, and in common emitter circuit the input is base current I_B and the output is collector current. So, beta is I_C by I_B and which is very high, and transistors with current gain 50, 80, 100, 200, 300 are commonly available in the market.

So, this was about the transistors. And then, we talked about the biasing which is the very important part of the transistor circuits. So, an amplifier will require the emitter junction to be forward bias, collector junction to be reverse bias and besides that, that will just saying this that, emitter is forward biased and collector is reverse biased is not sufficient, that requires a proper choice of the operating point. By choosing an operating point, we mean choosing dc collector current and dc drop across the junction V_{CE} . So, that is the proper choice of the operating point, operating point may shift because of three basic reasons temperature, aging, replacement of the device. So, we have to design a good circuit, a stable circuit. So, even if the parameter change, temperature changes or the device has worked for long life, so even then quiescent not vary.

And we had discussed the three schemes; the self biasing scheme, the emitter bias and the collector feedback bias. And these three schemes are widely used to design circuits. Depending on our requirements and facility available, any one of the three schemes can be picked up and the amplifier circuit can be designed. And so, that we discuss; we will continue our discussion further; and now, we move to the unit 3.